



Exercise 1


Calculate the resistor values required to bias a silicon **NPN** transistor in each of the two circuits shown below.

Given: $\beta = 100$, $V_{CC} = 10 \text{ V}$

It is desired that the quiescent operating point be fixed at:

$V_{CE0} = 5 \text{ V}$, $I_{C0} = 1 \text{ mA}$.

with: $V_{BE0} = 0.7 \text{ V}$

 

Exercise 2


An **NPN** silicon transistor is biased using a base voltage divider, as shown in the circuit diagram.

Given: $\beta = 100$ and $V_{CC} = 10 \text{ V}$

The desired operating point (bias point) is defined by:

$V_{CE0} = 5 \text{ V}$, $I_{C0} = 1 \text{ mA}$, $V_{BE0} = 0.7 \text{ V}$

1. Determine the Thevenin equivalent model between the base of the transistor and ground.
2. Deduce the equation of the input load line (base circuit load line).
3. Assuming that **RB1** is 100 times greater than **RB2**, calculate the values of the resistors **RB1** and **RB2**.
4. Derive the equation of the output load line.
5. Calculate the value of the collector resistor **Rc**

 

Exercise 3