

# Machine structure 2

Ghemougui Abdessettar

Computer Science Department  
University of Msila


2025

# Sequential Circuits


 
# The clock signal

- A clock pulse signal is a **square wave**. In a square wave, voltage varies by periodically switching from **high** to **low** state (no 'in between' values), it is therefore a **digital** signal as there are only two states.
- The **period**  $T$  of the clock pulse is the time in seconds taken for one complete **cycle**.
- The **frequency**  $f$  measured in hertz (Hz) of the clock cycle can be found by calculating the reciprocal of the period  $f = \frac{1}{T}$ .



# Flip flops


-  latches vs Flip flops
- Master slave D Flip-Flop
- Master-slave SR flip-flop
- JK-Flip flop
- JK timing diagram
- T-Flip Flop
- T Flip Flop timing diagram
- Asynchronous Set and Reset
- Interconversion of flip flops

# Latch synchronization problem

- Provide us with a simple form of memory.
- Latch circuit responds any time the inputs change.
- We want to limit the state change to a very narrow time period witch will allow us to synchronize the state change of several devices.

 
## D latch

- As long as the clock signal is high any change in the value of input  $D$  appears in the output  $Q$


 
## D Flip flop



- $Q$  changes only on the clock signal transition (rising edge) and the Flip flop is in latch state during all the clock cycle.





  
# latches vs Flip flops

- A latch is sensitive to the **level** of the clock.
- A flip-flop is sensitive to the **transition** of the clock
- A latch is called a **level-triggered** memory element
- A flip-flop is called an **edge-triggered** memory element



 
# Master slave D Flip-Flop (positive edge $\square$ )

- A **master-slave** D flip-flop can be built from two D latches.
- The master latch is enabled when the clock is low and the slave is disabled.
- The slave latch is enabled when the clock is high and the master is disabled.
- When the clock **transition** from low to high the value stored in the master latch gets stored in the slave latch.
- The outputs change on the **positive edge**  $\square$  of a pulse on the clock signal.



 
# Master slave D Flip-Flop (negative edge $\neg$ )

- The master latch is enabled when the clock is **high** and the slave is disabled.
- The slave latch is enabled when the clock is **low** and the master is enabled.
- When the clock **transition** from high to low the value stored in the master latch gets stored in the slave latch.
- The outputs change on the **negative edge**  $\neg$  of a pulse on the clock signal.




 
# Master-slave SR flip-flop (positive edge $\square$ )

- A **master-slave** SR flip-flop can be built from two SR latches.
- The master latch is enabled when the clock is low and the slave is disabled.
- The slave latch is enabled when the clock is high and the master is disabled.
- When the clock **transition** from low to high the value stored in the master SR latch gets stored in the slave SR latch.
- The outputs change on the **positive edge**  $\square$  of a pulse on the clock signal.


  
# Master slave SR Flip-Flop (negative edge $\neg$ )


- The master latch is enabled when the clock is **high** and the slave is disabled.
- The slave latch is enabled when the clock is **low** and the master is disabled.
- When the clock **transition** from high to low the value stored in the master SR latch gets stored in the slave SR latch.
- The outputs change on the **negative edge**  $\neg$  of a pulse on the clock signal.



# JK-Flip flop



The **JK-flip flop** represents an enhancement over the SR flip flop by addressing the issue of the forbidden state through the incorporation of feedback. The JK-Flip flop, originally named after its inventor, Jack Kilby

| E | J | K | Q      | $\bar{Q}$ | operation |
|---|---|---|--------|-----------|-----------|
| 0 | x | x | latch  | latch     | memory    |
| 1 | 0 | 0 | latch  | latch     | memory    |
| 1 | 0 | 1 | 0      | 1         | reset     |
| 1 | 1 | 0 | 1      | 0         | set       |
| 1 | 1 | 1 | toggle | toggle    | invert    |

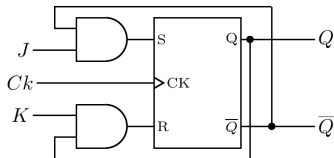

  
# Master slave JK Flip-Flop (negative edge $\neg$ )

- The master latch is enabled when the clock is **high** and the slave is disabled.
- The slave latch is enabled when the clock is **low** and the master is enabled.
- When the clock **transition** from high to low the value stored in the master SR latch gets stored in the slave SR latch.
- The outputs change on the **negative edge**  $\neg$  of a pulse on the clock signal.




# JK Flip-Flop (Characteristic table)

 


| J | K | $Q_n$ | $Q_{n+1}$ |
|---|---|-------|-----------|
| 0 | 0 | 0     | 0         |
| 0 | 0 | 1     | 1         |
| 0 | 1 | 0     | 0         |
| 0 | 1 | 1     | 0         |
| 1 | 0 | 0     | 1         |
| 1 | 0 | 1     | 1         |
| 1 | 1 | 0     | 1         |
| 1 | 1 | 1     | 0         |

# JK Flip-Flop (Excitation table)

 

| $Q_n$ | $Q_{n+1}$ | J | K |
|-------|-----------|---|---|
| 0     | 0         | 0 | x |
| 0     | 1         | 1 | x |
| 1     | 0         | x | 1 |
| 1     | 1         | x | 0 |

 
# JK timing diagram (positive edge $\square$ )



# T-Flip Flop


The **T-flip flop** is essentially a modification of the JK flip flop, where the J and K inputs are tied together and connected to the toggle input **T**. When the toggle input is activated, the output of the T latch changes state, toggling between its two possible states (0 and 1).

| E | T | Q      | $\bar{Q}$ | operation |
|---|---|--------|-----------|-----------|
| 0 | x | latch  | latch     | memory    |
| 1 | 0 | latch  | latch     | memory    |
| 1 | 1 | toggle | toggle    | invert    |

 

 
# T Flip-Flop

- T flip flop is known as **Toggle** Flip Flop because it can toggle (flip) its output depending on the input  $T$ .
- T here stands for Toggle.
- Toggle basically indicates that the output  $Q$  will be flipped either from 1 to 0 or from 0 to 1.
- if  $T$  is zero the flip flop will remain on memory state (latch state)
- if  $T$  is one during a clock transition the value of  $Q$  will flip.



 
# T Flip Flop timing diagram (positive edge $\neg$ )




 
# Asynchronous Set and Reset

- When Flip-Flops are powered, their initial state is **unknown**
- We can add asynchronous **Preset** and **Clear** inputs taht work independently of the clock.
- **Prset** forces Q to become immediately 1, independently of the clock.
- **Clear** forces Q to become immediately 0, independently of the clock.



# Asynchronous Set and Reset

  

# Interconversion of flip flops

To convert a flip flop of type X to a flip flop of type Y we follow these steps:

- fill the characteristic table of the target flip flop Y
- fill the excitation table of the source flip flop X
- Get the simplified expressions for each excitation input ( X inputs) as a function of Y inputs and the current state (use kmap if needed).
- Draw the circuit diagram of desired flip-flop according to the simplified expressions using given flip-flop and necessary logic gates

# Conversion of an S-R Flip-flop to a D Flip-flop

To convert SR flip flop to a D flip flop follow these steps:

- fill the characteristic table of the D flip flop.
- fill the excitation table of the SR flip flop.
- Get the simplified expressions for each excitation input ( SR inputs) as a function of D inputs and the current state (use kmap if needed).
- Draw the circuit diagram of desired flip-flop according to the simplified expressions using given flip-flop and necessary logic gates

# Conversion of an S-R Flip-flop to a D Flip-flop

1 D characteristic table

| D | $Q_n$ | $Q_{n+1}$ |
|---|-------|-----------|
| 0 | 0     | 0         |
| 0 | 1     | 0         |
| 1 | 0     | 1         |
| 1 | 1     | 1         |

2 SR excitation table

| $Q_n$ | $Q_{n+1}$ | S | R |
|-------|-----------|---|---|
| 0     | 0         | 0 | x |
| 0     | 1         | 1 | 0 |
| 1     | 0         | 0 | 1 |
| 1     | 1         | x | 0 |

SR to D conversion table

| D | $Q_n$ | S | R |
|---|-------|---|---|
| 0 | 0     | 0 | x |
| 0 | 1     | 0 | 1 |
| 1 | 0     | 1 | 0 |
| 1 | 1     | x | 0 |

$$R = \overline{D}$$

$$S = D$$

# Conversion of D Flip-flop to an SR Flip-flop

Table: SR  
characteristic table

| S | R | $Q_n$ | $Q_{n+1}$ |
|---|---|-------|-----------|
| 0 | 0 | 0     | 0         |
| 0 | 0 | 1     | 1         |
| 0 | 1 | 0     | 0         |
| 0 | 1 | 1     | 0         |
| 1 | 0 | 0     | 1         |
| 1 | 0 | 1     | 1         |
| 1 | 1 | 0     | x         |
| 1 | 1 | 1     | x         |

Table: D excitation  
table

| $Q_n$ | $Q_{n+1}$ | D |
|-------|-----------|---|
| 0     | 0         | 0 |
| 0     | 1         | 1 |
| 1     | 0         | 0 |
| 1     | 1         | 1 |

Table: D to SR  
conversion table

| S | R | $Q_n$ | $Q_{n+1}$ | D |
|---|---|-------|-----------|---|
| 0 | 0 | 0     | 0         | 0 |
| 0 | 0 | 1     | 1         | 1 |
| 0 | 1 | 0     | 0         | 0 |
| 0 | 1 | 1     | 0         | 0 |
| 1 | 0 | 0     | 1         | 1 |
| 1 | 0 | 1     | 1         | 1 |
| 1 | 1 | 0     | x         | x |
| 1 | 1 | 1     | x         | x |

# Conversion of D Flip-flop to an SR Flip-flop

Table: D to SR conversion table

| S | R | $Q_n$ | $Q_{n+1}$ | D |
|---|---|-------|-----------|---|
| 0 | 0 | 0     | 0         | 0 |
| 0 | 0 | 1     | 1         | 1 |
| 0 | 1 | 0     | 0         | 0 |
| 0 | 1 | 1     | 0         | 0 |
| 1 | 0 | 0     | 1         | 1 |
| 1 | 0 | 1     | 1         | 1 |
| 1 | 1 | 0     | x         | x |
| 1 | 1 | 1     | x         | x |

|       |   |    |    |    |    |
|-------|---|----|----|----|----|
|       |   | SR |    |    |    |
|       |   | 00 | 01 | 11 | 10 |
| $Q_n$ | 0 |    |    | x  | 1  |
|       | 1 | 1  |    | x  | 1  |

$$D = S + \bar{R}Q_n$$

