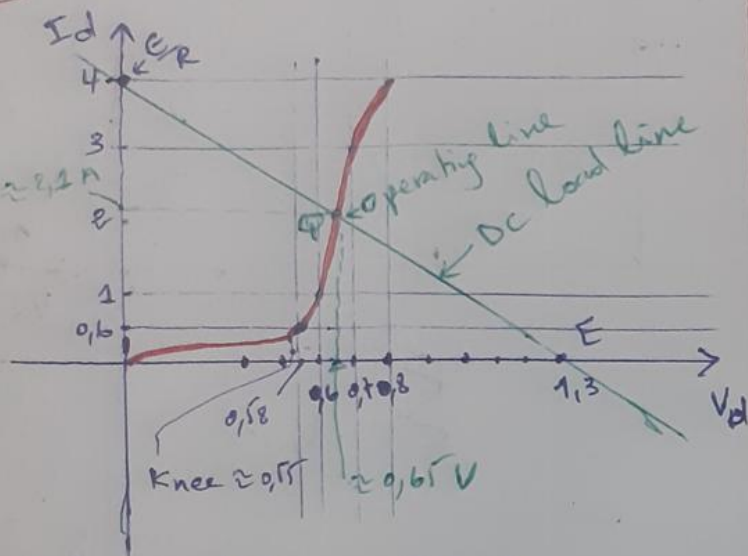


Solution of Series 3

Exercise 1

1) Trace the characteristic of this diode




2) $\frac{1}{R_d} = \frac{\Delta I_d}{\Delta V_d} = \frac{3 - 0.6}{0.7 - 0.58} = 20$

$R_d = \frac{1}{20} = 0.05 \Omega$

3) Determine the knee voltage V_0

$V_0 \approx 0.58 \text{ V}$

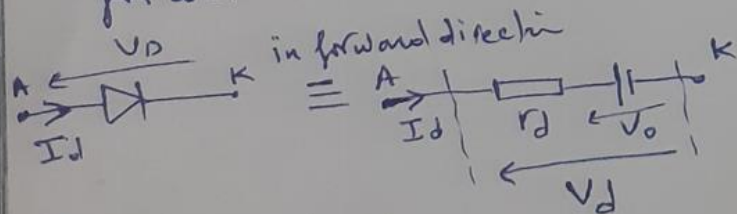4) Give the equivalent electrical diagram of this diode in the forward direction.



5) V_{dmax} and I_{dmax}

$P_d = V_d \cdot I_d$

$P_{dmax} = V_{dmax} \cdot I_{dmax}$

$V_{dmax} = V_0 + R_d \cdot I_{dmax}$

$P_{dmax} = (V_0 + R_d I_{dmax}) \cdot I_{dmax}$
 $\uparrow \quad \quad \uparrow \quad \quad \uparrow$
 $3 \quad \quad 0.58 \quad \quad 0.05$

$0.05 I_{dmax} + 0.58 I_{dmax} = 3 = 0$

$\Delta = (0.58)^2 + 4 \cdot 0.05 \cdot 3 = 0.9$


$I_{dmax1} = \frac{-0.58 - \sqrt{\Delta}}{2 \cdot 0.05} = -15 \text{ A} \times$

$I_{dmax2} = \frac{-0.58 + \sqrt{\Delta}}{2 \cdot 0.05} = 4 \text{ A} \checkmark$

So $I_{dmax} = 4 \text{ A}$

$V_{dmax} = R_d I_{dmax} + V_0$

$V_{dmax} = 0.25 \text{ V}$

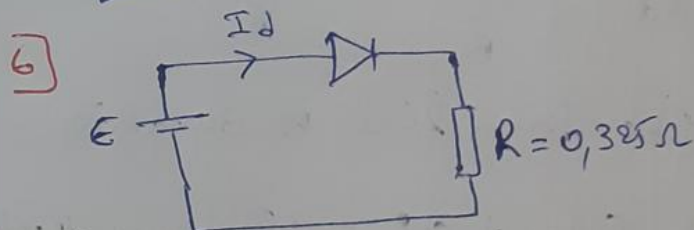

→ Determine the value of E so that the DC load line passes through the point $M(0 \text{ V}, 4 \text{ A})$

$E = R I_d + V_d$

$\Rightarrow I_d = \frac{E}{R} - \frac{V_d}{R}$

DC load line

for $(I_d = 4 \text{ A})$ and $(V_d = 0) \Rightarrow$

$E = 4 \cdot 0.325 + 0 = 1.3 \text{ V}$

→ Operating point

The operating point of a diode is the point of intersection between the DC load line and the diode's characteristics curve.

• The equation of DC line is

$$I_d = \frac{E}{R} - \frac{V_d}{R}$$

if $V_d = 0 \Rightarrow I_d = \frac{E}{R} = 4 \text{ A}$

if $I_d = 0 \Rightarrow V_d = E = 1,3 \text{ V}$

$Q(2,1 \text{ A}, 0,65 \text{ V})$

$\boxed{7} \Delta E = e(t); e(t) = 0,2 \sin(\omega t)$

$$I_d = \frac{E + e(t)}{R} - \frac{V_d}{R}; e(t) = 0,2 \sin(\omega t)$$

⇒ the load line is dynamic


$$V_d = \begin{cases} 1,3 + 0,2 = 1,5 \text{ V} & \text{maximal value} \\ 1,3 - 0,2 = 1,1 \text{ V} & \text{min value} \end{cases}$$

$$I_d = \begin{cases} \frac{E + e}{R} = \frac{1,3 + 0,2}{0,325} = 4,61 \text{ A} \\ \frac{E - e}{R} = \frac{1,3 - 0,2}{0,325} = 3,38 \text{ A} \end{cases}$$

$$\frac{1}{R_d} = \frac{\Delta I_d}{\Delta V_d}$$


$$\frac{i_d(\omega)}{V_d(\omega)} = \frac{1}{R_d}$$

$$\Rightarrow i_d(\omega) = \frac{1}{R_d} V_d(\omega)$$

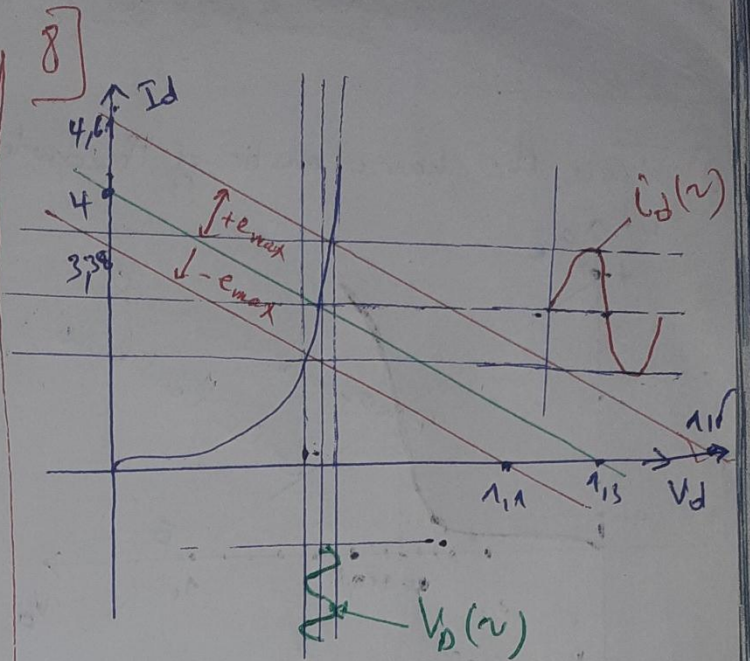

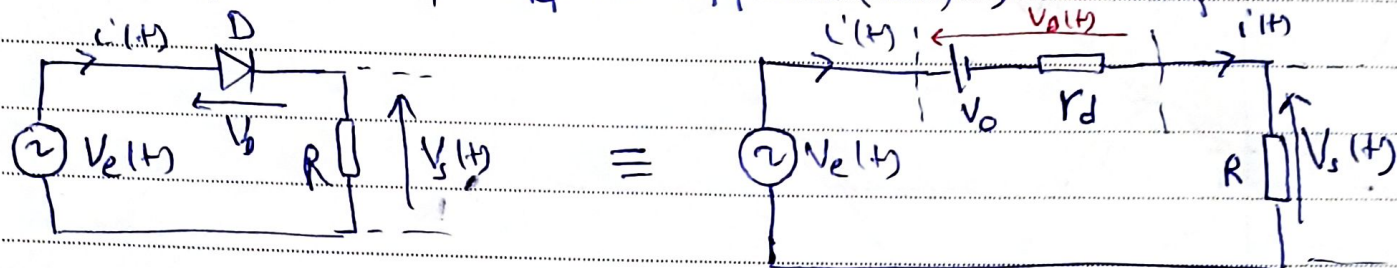Exercise 2 :

$$V_0 = 0.5 \text{ V}, R_d = 5 \Omega, V_e(t) = V_m \sin(\omega t); \omega = 2\pi f$$



1. Determine the expressions for the current $i(t)$ and the voltage $V_D(t)$.

→ The diode D is reverse-biased if $V_e \leq V_0 \Rightarrow i(t) = 0$

→ The diode D is forward-biased if $V_e > V_0 \Rightarrow i(t) \neq 0$

* Applying the Kirchhoff's law (VKL)

$$V_e(t) = V_0 + (R_d + R)i(t) \Rightarrow i(t) = \frac{V_e(t) - V_0}{(R + R_d)}$$

$$V_D(t) = V_e(t) - V_0(t) = V_e(t) - R i(t)$$

$$V_D(t) = \begin{cases} V_e(t) & \text{if } i(t) = 0 \quad \text{D is reverse-biased} \\ V_e(t) - R i(t) & \text{if } i(t) \neq 0 \quad \text{D is forward-biased} \end{cases}$$


$$V_D(t) = V_e(t) - R i(t) = V_e(t) - R \cdot \frac{V_e(t) - V_0}{(R + R_d)}$$

$$V_D(t) = \frac{R_d V_e(t) + R V_0}{(R + R_d)}$$

$$V_D(t) = \frac{R_d}{R + R_d} V_e(t) + \frac{R}{R + R_d} V_0 \quad ; \text{ if } R_d \ll R \Rightarrow V_D(t) \approx V_0$$

$$V_D(t) = \begin{cases} V_e(t) & \text{if } i(t) = 0 \quad \text{D is reverse-biased} \\ \frac{R_d}{R_d + R} V_e(t) + \frac{R}{R_d + R} V_0 \approx V_0 & \text{if } i(t) \neq 0 \quad \text{D forward-biased} \end{cases}$$

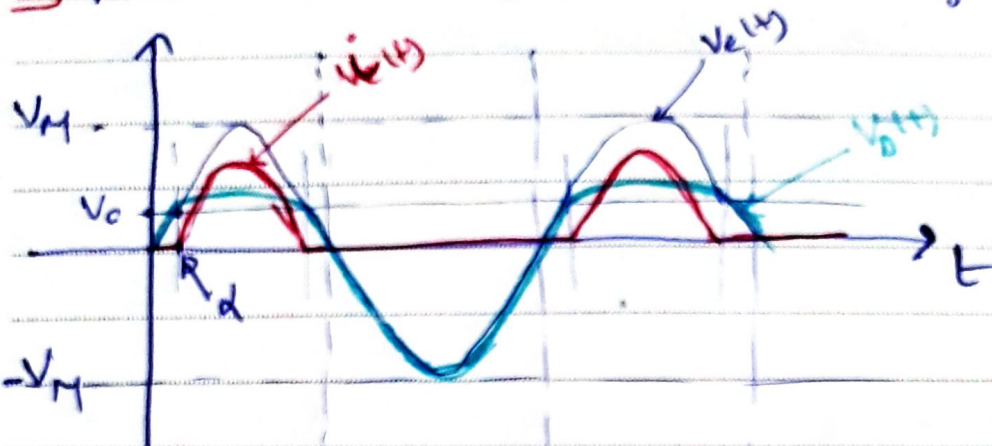2] Plot $i(t)$ and $V_o(t)$ on the same graph



3] Calculate the firing angle α ; for $V_M = 2V_o$ then $V_M = 10V$

$$V_o(\alpha) = V_o = V_M \sin(\alpha) \quad (\Rightarrow) \quad \sin \alpha = \frac{V_o}{V_M}$$

$$\alpha = \arcsin\left(\frac{V_o}{V_M}\right)$$

$$\rightarrow \text{For } V_M = 2V_o \Rightarrow \alpha = \arcsin\left(\frac{V_o}{2V_o}\right) = \arcsin\left(\frac{1}{2}\right)$$

$$\alpha = \frac{\pi}{6} = 0,52 \text{ rad}$$

$$\rightarrow \text{For } V_M = 10V \Rightarrow \alpha = \arcsin\left(\frac{V_o}{10}\right) = \arcsin\left(\frac{0,5}{10}\right)$$

$$\alpha = 0,05 \text{ rad}$$


4] Compare the values (Silicon - Germanium)

$$\begin{aligned} \rightarrow \text{For } V_M = 2V_o &\Rightarrow \alpha = 0,52 \text{ rad} \\ \rightarrow \text{For } V_M = 10V &\Rightarrow \alpha = 0,03 \text{ rad} \end{aligned} \quad \left. \vphantom{\begin{aligned} \rightarrow \text{For } V_M = 2V_o \\ \rightarrow \text{For } V_M = 10V \end{aligned}} \right\} \text{Germanium}$$

→ We notice that the change of the diode has almost no influence on the the firing angle.


→ For a good rectification, we have an interest in taking $V_M \gg V_o$.

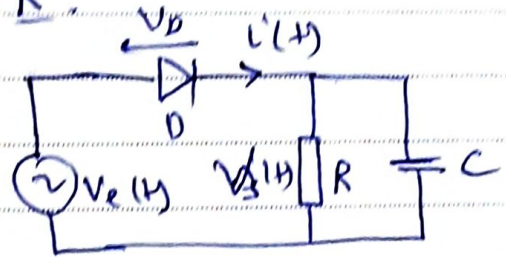5] Explain what happens when a capacitor C connected in parallel with the resistor R .



When a capacitor C is connected in parallel to the resistor R , the capacitor charges when the diode is forward-biased, up to the voltage $(V_H - V_0)$ (because $V_H = V_e(t) - V_0(t)$), and when the diode is reverse-biased (if $V_e(t) < V_H - V_0$), the capacitor discharges through the resistor R .


6] Plot the curve $i(t)$ in this case.

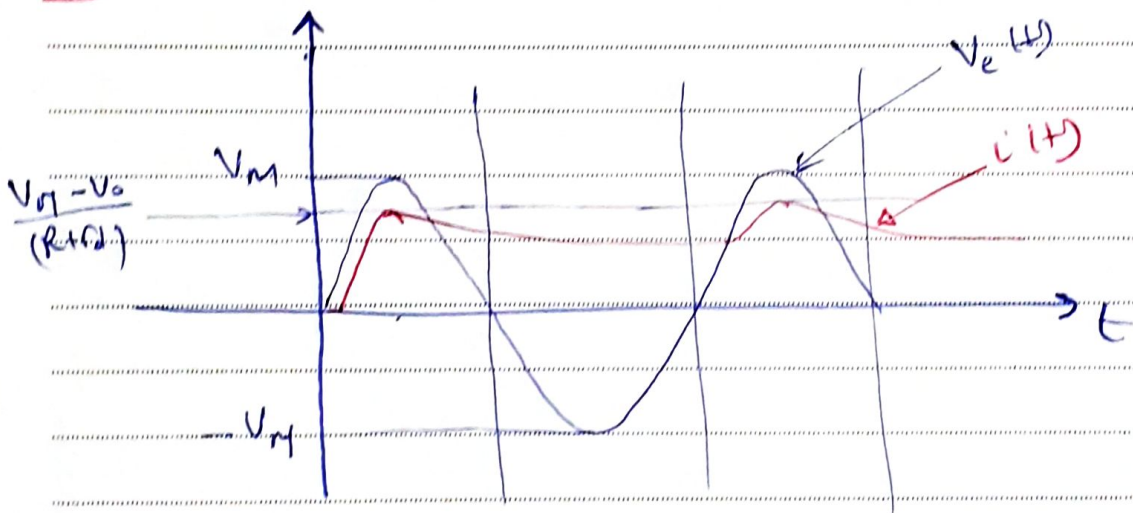

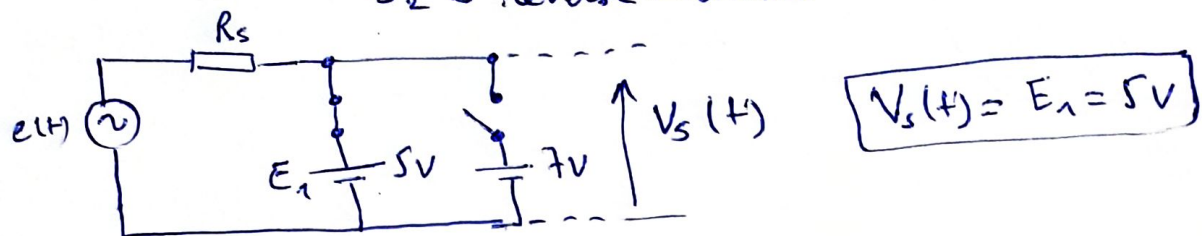Exercise N°3

1- Determine ^{then} ~~and~~ plot the output $V_s(t)$ of the circuit-
 $E_1 = 5V$, $E_2 = 7V$, $V_e(t) = 12 \sin(\omega t)$

* If $V_e(t) < 0$: D_1 is forward-biased
 D_2 is reverse-biased




* If $V_e(t) > 0$

* If $V_e(t) < 5V$: D_1 is forward-biased
 D_2 is reverse-biased


$$V_s(t) = E_1 = 5V$$

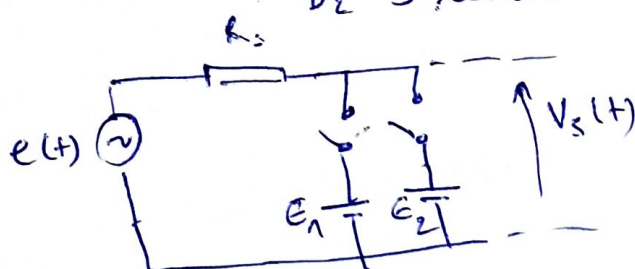* If $5V < V_e(t) < 7V$: D_1 is reverse-biased
 D_2 is reverse-biased




$$V_s(t) = V_e(t)$$

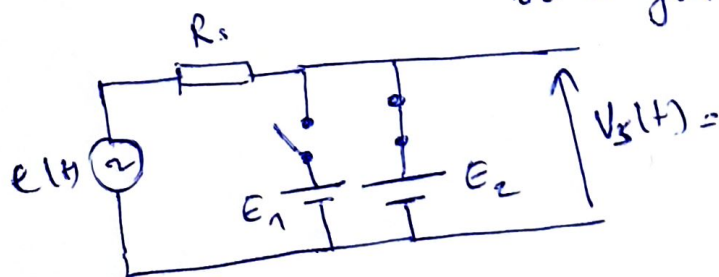* If $V_e(t) > 7V$: D_1 is reverse-biased
 D_2 is forward-biased



$$V_s(t) = E_2 = 7V$$

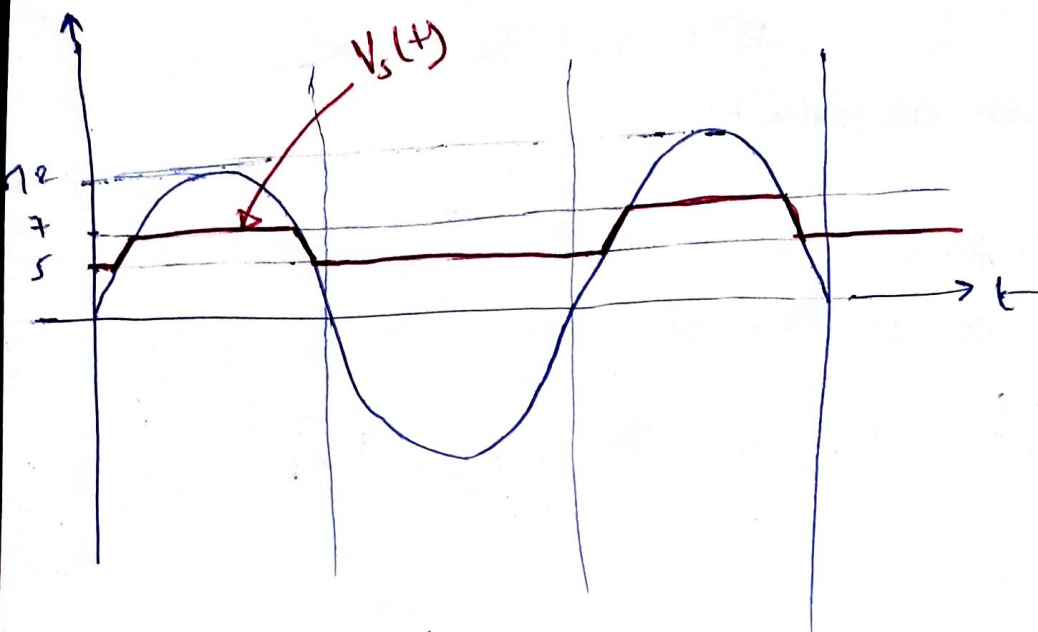

Transfer characteristic $V_s = \frac{2}{7}(V_e)$

