

جامعة محمد بوضياف- المسيلة -
Mohamed Boudiaf University at M'sila
كلية التكنولوجيا
Faculty of Technology
قسم الهندسة الكهربائية
Department of Electrical Engineering

University year: 2025/2026

2nd year Electrical Engineering

Applied Work in Electrical and Electronic Measurements

السنة الجامعية : 2026/2025

السنة الثانية هندسة كهربائية

أعمال تطبيقية في القياسات الكهربائية والإلكترونية

PW n°01 : Resistance measurement

Duration : 1^h30.

Date of the experiment: / /

Report prepared by:

Last Name	First Name	Group	S/Group	Final Note
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-

Instructions :

- Internal laboratory regulations must be observed.
- You must wear a lab coat.
- Attendance is compulsory and will be monitored. Any unjustified absence or failure to hand in a report will result in a mark of 0/20.
- Have your assemblies checked before connecting the voltage source.
- It is strictly forbidden to move equipment from one station to another. In the event of a breakdown or faulty equipment, contact the teacher.
- The report must be written by a maximum of four students.
- The report must be handed in at the beginning of the next session.
- The report must include the following sections:
 - TP cover page.
 - The date of the practical session.
 - Last Name and first name of the main writer.
 - Last Names and first names of the WP participants.
 - Preparation and work in manuscript.

I. Aim of the manipulation

- ✓ Measure the unknown resistances using the following methods: Colour Code; Ohm Meter; Volt-Amperometric.
- ✓ Evaluate the absolute and relative accuracy of each method.

II. Equipment used

- Power Sources (DC).
- Resistors.
- Instruments (voltmeters, miliammeter, microammeter, multimeters).

III. Evaluation method

Continuous assessment: 100%.

IV. Theoretical reminder

A resistor is an electronic or electrical component whose primary characteristic is to resist the flow of electric current, measured in ohms. Electrical resistance is a fundamental part of electricity. The term "resistance" primarily refers to a physical property, but it has also come to refer to a specific type of component. Some people prefer to call it a "resistive device".

V. Method n°01: Direct measurements using Color Code Designation

To determine the ohmic value of a resistor, it is necessary to identify the colour bands present on the resistor (see Figure 1) and associate them with the universal colour code. The international standard IEC 60757, entitled "Colour Code Designation" (1983), defines a colour code to be applied to resistors to indicate their resistance values.

0 1 2 3 4 5 6 7 8 9 0 Black 1 Brown 2 Red 3 Orange 4 Yellow 5 Green 6 Blue 7 Purple 8 Grey 9 White ±1% Brown ±2% Red ±5% Gold ±10% Silver	±1% ±2% ±5% ±10% 27K EXAMPLE 0 X1 1 1 X10 2 2 X100 3 3 X1000 4 4 X10000 5 5 X100000 6 6 X1000000 7 7 X10000000 8 8 X100000000 9 9 X1000000000 +10 +100 4 Band Resistors	±1% ±2% ±5% ±10% 15K EXAMPLE 0 0 X1 1 1 1 X10 2 2 2 X100 3 3 3 X1000 4 4 4 X10000 5 5 5 X100000 6 6 6 X1000000 7 7 7 X10000000 8 8 8 X100000000 9 9 9 X1000000000 +10 +100 5 Band Resistors	Temperature Coefficient ±1% 100 50 ±2% 25 15 ±5% 10 5 ±10% 1 620K EXAMPLE 0 0 X1 1 1 1 X10 2 2 2 X100 3 3 3 X1000 4 4 4 X10000 5 5 5 X100000 6 6 6 X1000000 7 7 7 X10000000 8 8 8 X100000000 9 9 9 X1000000000 +10 +100 6 Band Resistors
Color Codes	4 Band Resistors	5 Band Resistors	6 Band Resistors

Figure 1: Resistor Color Code

PW n°01: Resistance measurement



$R_1 =$

$\Delta R_1 =$



$R_2 =$

$\Delta R_2 =$

VI. Method n°02 : Direct measurements using the ohmmeter

Measure the values of resistors R_1 , and R_2 using the multimeter in ohmmeter mode, then calculate the relative ∂R and absolute ΔR uncertainties using the following relationship:

$$\Delta R = R * \text{precision} + \text{number of digits} * \text{resolution}$$

Instructions for recording the accuracy of the measurements provided according to the range used are given in the uncertainty table below:

Range	Precision + Number of digits	Resolution	Uncertainty
200 Ω	$\pm(1\% + 3 \text{ digits})$ 0,1 Ω	0,1 Ω	4,5 Ω
2k Ω	(0,8%+1digits)	1 Ω	30 Ω
20k Ω	$\pm(0,8\% + 1 \text{ digits})$	10 Ω	300 Ω
200k Ω	$\pm(0,8\% + 1 \text{ digits})$	100 Ω	3k Ω
2M Ω	$\pm(0,8\% + 1 \text{ digits})$	1k Ω	42k Ω
20M Ω	$\pm(2\% + 2 \text{ digits})$	10k Ω	620k Ω

Table 1

Measure the resistances, then calculate the measurement uncertainty and complete the following table

	Measurement of $R_1 = 220\Omega$	Measurement of $R_2 = 220K\Omega$
Range		
R		
ΔR		
$\partial R = \Delta R / R$		

Table 2

VII. Method n°03 : Indirect measurements using the Volt-Amperometric method

1) Selecting the appropriate circuit

This involves selecting the appropriate circuit, upstream or downstream, for measuring each of the resistors R_1 and R_2 resistors, specifying the measuring equipment. Then, once the measurements have been made, determine the value of each resistor and its uncertainty for the selected circuit.

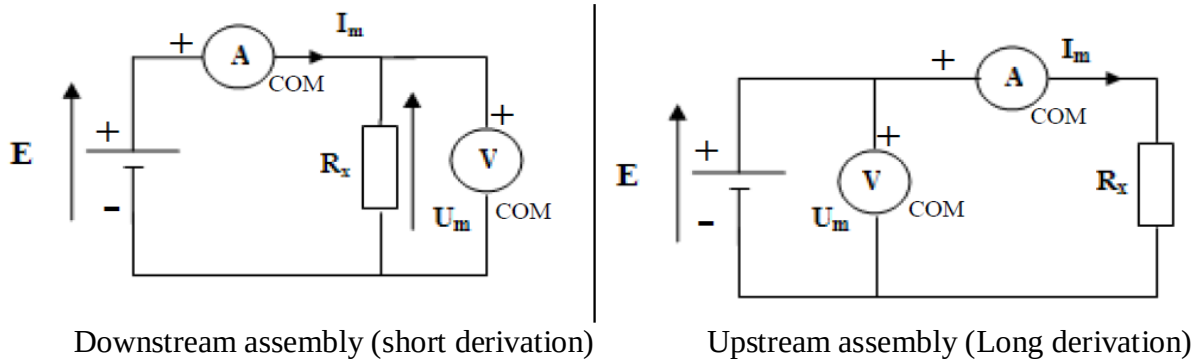


Figure 2

The choice of the assembly is made according to the following rule:

If $R \leq \sqrt{R_A * R_V}$ (low value resistances), we prefer the short assembly;

If $R \geq \sqrt{R_A * R_V}$ (high value resistances), we prefer the long assembly;

2) Measurement Table

$E=5V$,

Miliammeter Class =.....

Microammeter Class =.....

Voltmeter Class =.....

3) Remarks

✚ **Absolute uncertainty ΔX :** Calculation of the absolute uncertainty ΔX due to a measuring device

$$\Delta X = \frac{\text{Class} * \text{Rang}}{100}$$

✚ **Relative uncertainty:** $\partial X = \Delta X / X$ generally expressed as a percentage (%).

$$\Delta R / R = \Delta I / I + \Delta V / V$$

PW n°01: Resistance measurement

- Measure the current and voltage for the two resistors R_1 , R_2 .
- Record the measured and calculated results in the table below:

	$R_1=220\Omega$	$R_1=220\Omega$	$R_2=220K\Omega$	$R_2=220K\Omega$
Assembly adopted	Downstream	Upstream	Downstream	Upstream
Range for I (C_A)				
Scale for I (E_A)				
Current reading (L_A)				
$I_m=(L_A *C_A/E_A)$				
Range for V(C_V)				
Scale for V (E_V)				
Voltage reading (L_V)				
$U_m= (L_V *C_V/E_V)$				
$R_m=U_m/I_m$				
ΔR_m				

Table 3

Interpretation of results

.....

.....

.....

VIII. Conclusion

.....

.....

.....

.....