

University year: 2025/2026

السنة الجامعية : 2026/2025

2nd year Electrical Engineering

السنة الثانية هندسة كهربائية

Applied Work in Electrical and Electronic Measurements

أعمال تطبيقية في القياسات الكهربائية والإلكترونية

PW n°02: Inductance measurement

Duration: 1^h30.

Date of the experiment: / /

Report prepared by:

Last Name	First Name	Group	S/Group	Final Note
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-

Instructions :

- Internal laboratory regulations must be observed.
- You must wear a lab coat.
- Attendance is compulsory and will be monitored. Any unjustified absence or failure to hand in a report will result in a mark of 0/20.
- Have your assemblies checked before connecting the voltage source.
- It is strictly forbidden to move equipment from one station to another. In the event of a breakdown or faulty equipment, contact the teacher.
- The report must be written by a maximum of four students.
- The report must be handed in at the beginning of the next session.
- The report must include the following sections:
 - TP cover page.
 - The date of the practical session.
 - Last Name and first name of the main writer.
 - Last Names and first names of the WP participants.
 - Preparation and work in manuscript.

I. Aim of the manipulation

- ✓ Measure an inductance using the volt-amperometric and series RLC methods.
- ✓ Measure Quality factor

II. Equipment used

- Power Sources (DC).
- The Oscilloscope
- Function Generator (GBF)
- Electrical loads (resistors, inductors and capacitors).
- Measuring instruments (multimeters, ammeters, milliammeters, voltmeters).

III. Evaluation method

Continuous assessment: 100%.

IV. Theoretical reminder:

A coil consists of a winding of conductive turns around an insulator. It therefore has a certain internal resistance due to the long length of wire. The coil is therefore symbolised in the receiver convention as follows:

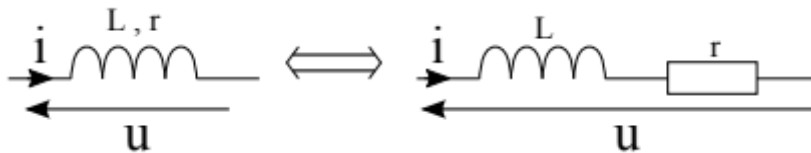


Figure 1: Symbolisation of a real coil, receiver convention

V. Method n°01: Indirect measurements using the Volt-Amperometric method

1) Volt-Amperometric method with DC source

- Carry out the following assembly.

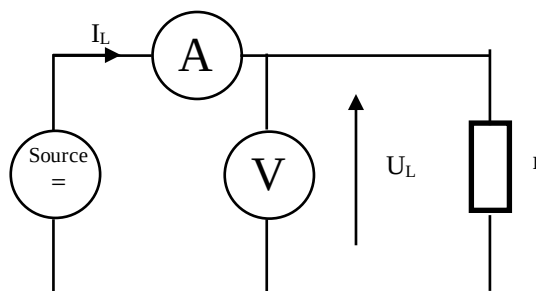


Figure 2: Volt-Amperometric method with DC source

PW n°02: Inductance measurement

- Find U_L and I_L by varying U from $1V$ to $9V$.

$U(V)$	1	3	5	7	9
$U_L(V)$					
$I_L(A)$					
$Z = r = U_L / I_L$					
r_{moy}					

Table 1

2) Volt-Amperometric method with AC source

- The coil is fed by a sinusoidal generator $U(t)$ with an effective value $U(t) = 7V$ and a variable frequency.
- Carry out the installation by positioning the equipment so that $U_L(V)$, I_L

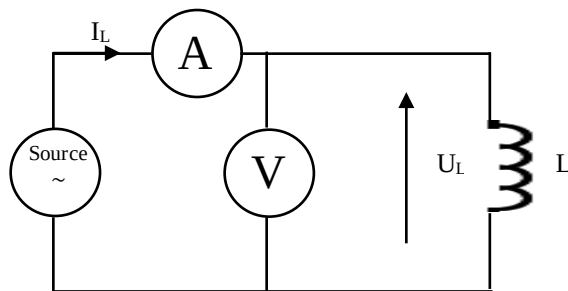


Figure 3: Volt-Amperometric method with AC source

- Find $U_L(V)$, I_L by varying the frequency from **100 Hz to 250 Hz**
- Calculate the value of Z from these measurements,
- Derive L

$f(Hz)$	100	150	200	250
$U_L(V)$				
$I_L(A)$				
$Z = U_L / I_L$				
$L (mH)$				

Table 2

VI. Method n°02: Indirect measurements using the Resonance of a series RLC circuit.

1) The Resonance of a series RLC circuit

To study the resonance of the RLC circuit, we will make the following series circuit:

- An inductor set at **150 mH**
- A capacitor set at **3.3 μF**
- A resistor set at **560 Ω** .


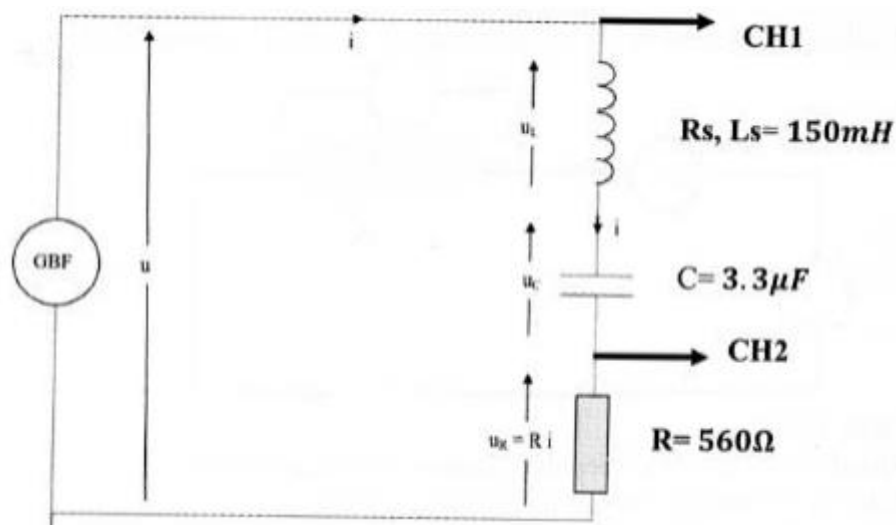


Figure 4: RLC circuit

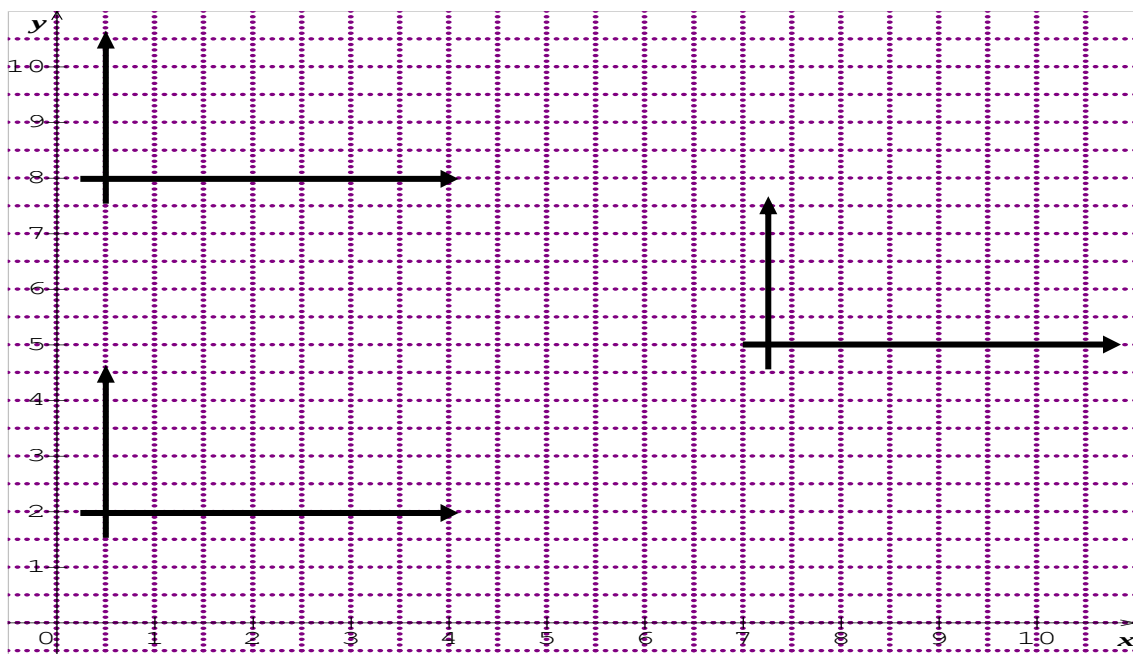- Look at the current and voltage curves on the oscilloscope.
- Plot these curves on a millimetre sheet for $f=100$; $f=225$; $f=500$.



PW n°02: Inductance measurement

- Calculate the phase shift $\varphi_{\text{experimental}}$ directly on the oscilloscope and compare it with the theoretical value.


.....

.....

.....

In general the impedance Z of a dipole is given by the relationship: $Z = U_{\text{max}} / I_{\text{max}} = U_{\text{eff}} / I_{\text{eff}} = U / I$ through the dipole.

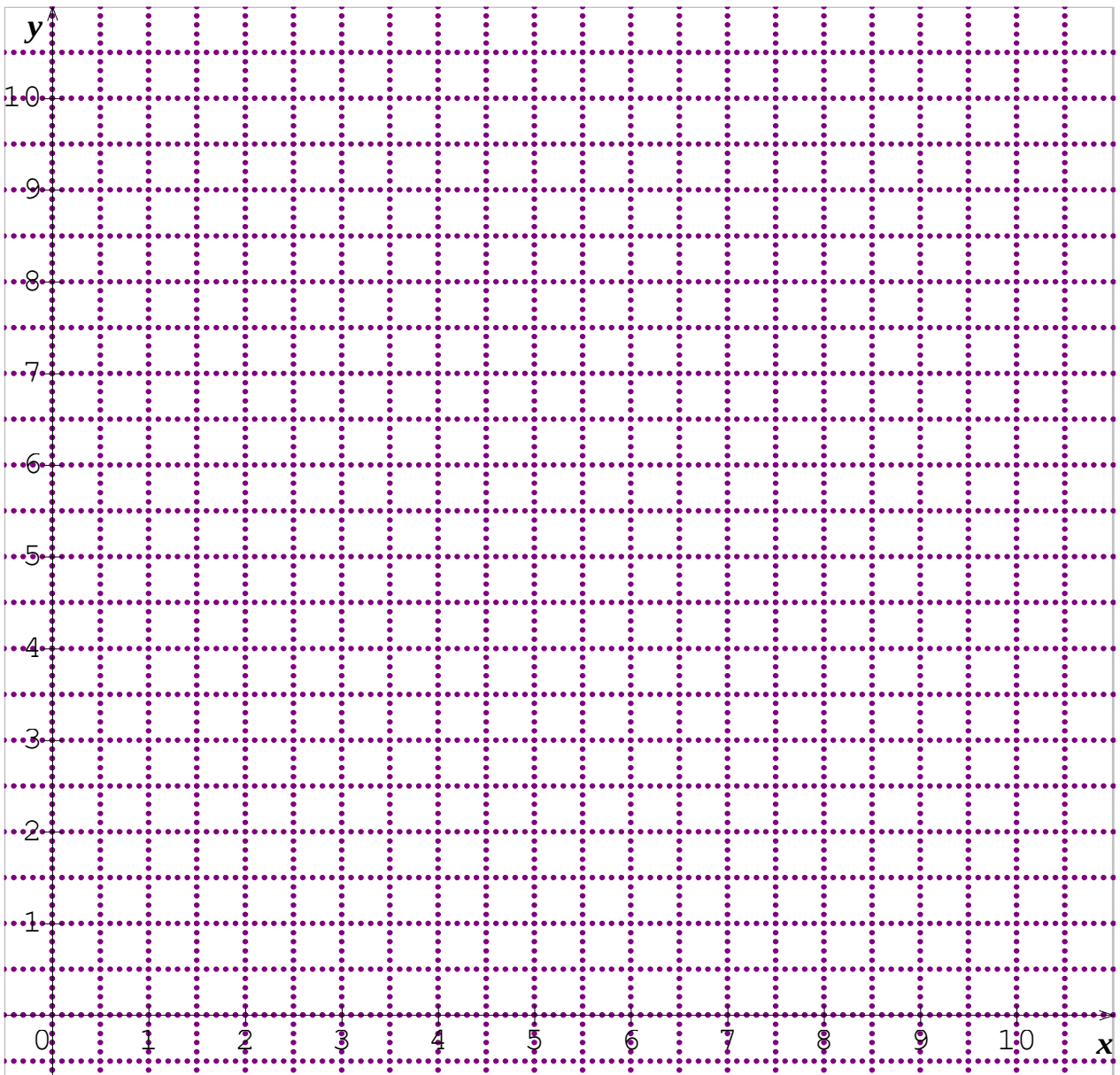- Record the amplitude of the voltage across the resistor U_R , the capacitor U_C and the coil U_L and the current I for frequencies between **100 Hz** and **500 Hz**.
- Plot the curves I , U_C , U_L , $U_R = G(f)$



PW n°02: Inductance measurement

- Calculate the resonance frequency
.....
- Calculate the bandwidth and the quality factor, given that $Q = f_0/\Delta f$
.....
.....
- Deduce the value of L for all frequencies;

f(Hz)	100	200	f_0	250	500
I (A)					
$U_R(V)$					
$U_C(V)$					
$U_L(V)$					
$Z = U / I$					
$R = U_R / I$					
$Z_C = U_C / I$					
$Z_L = U_L / I$					
L (mH)					

Table 3

- Discuss each of the results obtained.
.....
.....
.....

VII. Conclusion

.....
.....
.....
.....
.....
.....
.....