

## Solution of First series of exercises

### Exercise 1:

Exercise 1 :


1] Number of nodes : Two nodes (A and B)

\* Number of branches : Three branches

(AB, AFEB and ADCB)

\* Number of meshes : Three meshes

(ABCD, ABFEFA and DCBEFAD)

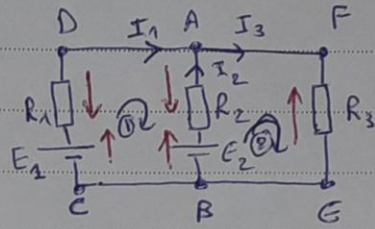

2] The application of Kirchhoff's laws

\* Kirchhoff's current law (KCL)

$$I_1 + I_2 = I_3 \quad (1)$$

\* Kirchhoff's voltage law (KVL)

$$\text{From mesh 1 : } E_1 - R_1 I_1 + R_2 I_2 - E_2 = 0 \quad (2)$$

$$\text{From mesh 2 : } E_2 - R_2 I_2 - R_3 I_3 = 0 \quad (3)$$

3] Determine  $I_1$ ,  $I_2$ ,  $I_3$  with :  $R_1 = 2\Omega$ ,  $R_2 = 5\Omega$ ,  $R_3 = 10\Omega$ ,  $E_1 = 20V$ ,  $E_2 = 70V$

$$\text{① and ② becomes } \begin{cases} 20 - 2I_1 + 5I_2 - 70 = 0 & \Rightarrow I_1 = -25 + 2.5I_2 \quad (4) \\ 70 - 5I_2 - 10I_3 = 0 & \xrightarrow{\text{implies that}} I_3 = 7 - 0.5I_2 \quad (5) \end{cases}$$

Replacing ④ and ⑤ in ①  $\Rightarrow \boxed{I_2 = 8A}$


Replacing the value of  $I_2$  in ④ and ⑤

$$\Rightarrow \boxed{I_1 = -5A} \quad \text{and} \quad \boxed{I_3 = 3A}$$

## Exercise 2:

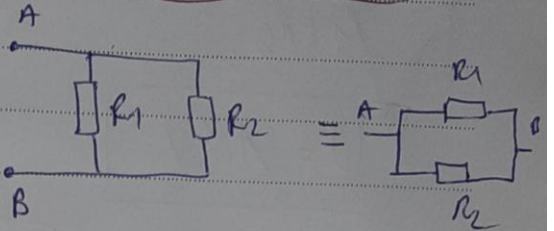1)

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad ; \quad R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$



$$AN: R_{eq} = \frac{14}{9} = 1,55 \Omega$$

2)  $V_g = R_{eq} \cdot i \Rightarrow i = \frac{V_g}{V_{eq}} \Rightarrow i = 11,57 A$

3) We use the current divider.

$$I_j = \frac{\frac{1}{R_j}}{\sum_{k=1}^n \frac{1}{R_k}} \cdot I$$

$$I_1 = \frac{1/R_1}{1/R_1 + 1/R_2} I = \frac{R_2}{R_1 + R_2} I \Rightarrow I_1 = 2,57 A$$

$$I_2 = \frac{1/R_2}{1/R_2 + 1/R_1} I = \frac{R_1}{R_1 + R_2} I \Rightarrow I_2 = 9 A$$

## Exercise 3:

By applying the voltage divider, determine the current  $i$  and the voltage  $u$ .



$$E = 6V, R_1 = 100\Omega, R_2 = R_3 = R_4 = 30\Omega$$

*Solu*

$$R_5 = R_2 + R_4 \Rightarrow R_5 = 100\Omega$$

$$R_6 = R_3 \parallel R_5 \Rightarrow R_6 = 33,3\Omega$$


$$= \frac{R_3 \cdot R_5}{R_3 + R_5}$$

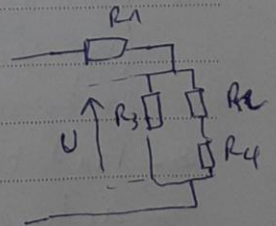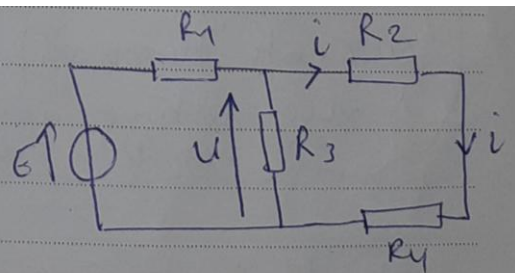



$$U = \frac{R_6}{R_1 + R_6} \cdot E$$

$$U = 1,5 \text{ V}$$

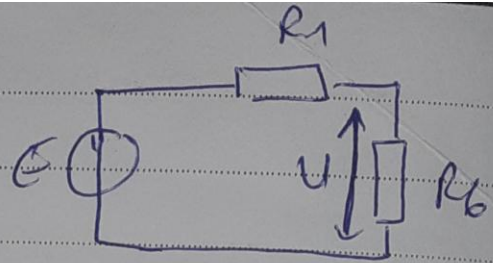

$$i = \frac{U}{R_5}$$

$$i = \frac{1,5}{100} = 15 \text{ mA}$$

#### Exercise 4:

##### Exercise 4:

1) Voltage divider

$$V_1 = \frac{R_1}{R_1 + R_2} E = \frac{1}{1+2} \cdot 3 = 1 \text{ V}$$

$$V_2 = \frac{R_2}{R_1 + R_2} E = \frac{2}{2+1} \cdot 3 = 2 \text{ V}$$

2) Current divider

$$I_1 = \frac{\frac{1}{R_1}}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2 + (R_3 \parallel R_4)}\right)} I = \frac{R_2 + (R_3 \parallel R_4)}{R_1 + R_2 + (R_3 \parallel R_4)} I = \frac{R_2 + \frac{R_3 R_4}{R_3 + R_4}}{R_1 + R_2 + \frac{R_3 R_4}{R_3 + R_4}} I$$

$$I_1 = 3,63 \text{ A}$$

$$I_2 = \frac{\frac{1}{R_2 + (R_3 \parallel R_4)}}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2 + (R_3 \parallel R_4)}\right)} I = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} I = \frac{R_1}{R_1 + R_2 + \frac{R_3 R_4}{R_3 + R_4}} I$$

$$I_2 = 1,36 \text{ A}$$


$$I_3 = \frac{R_4}{R_3 + R_4} I_2 = 0,9 \text{ A}$$

$$I_4 = \frac{R_3}{R_3 + R_4} I_2 = 0,45 \text{ A}$$

## Exercise 5:

**Exercise 5:**


**For  $i=0$  (Open circuit)**

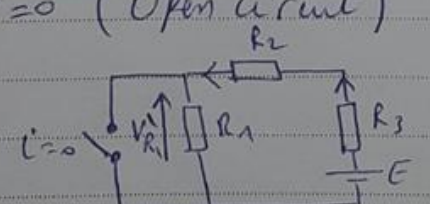

$V_{R_1}^I = \frac{R_1}{R_1 + R_2 + R_3} E$  (Voltage divider)

AN:  $V_{R_1}^I = 7.5V$

**For  $E=0$  (Short circuit)**

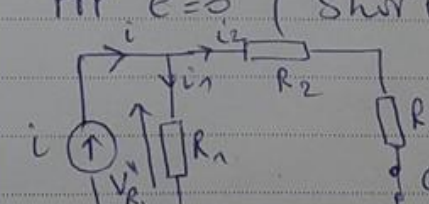


$i_1 = \frac{R_2 + R_3}{R_1 + R_2 + R_3} i$  (Current divider)

AN:  $i_1 = 0.5mA$   $V_{R_1}^{II} = R_1 \cdot i_1$   
 $V_{R_1}^{II} = 5V$

$V_{R_1}^I$  and  $V_{R_1}^{II}$  are in the same direction  $\Rightarrow$   $V_{R_1} = V_{R_1}^I + V_{R_1}^{II} = 12.5V$

## Exercise 6:

**Solution**

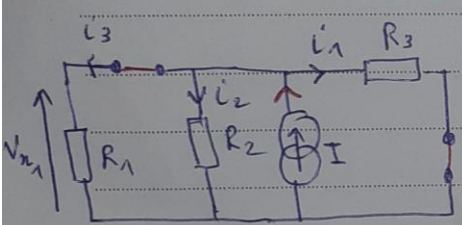


$V_{x1} = R_1 \cdot i_3$

$i_3 = \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3} I$

$= \frac{1}{1/1 + 1/3 + 1/6} 2$


$V_{x1} = 1.33V$

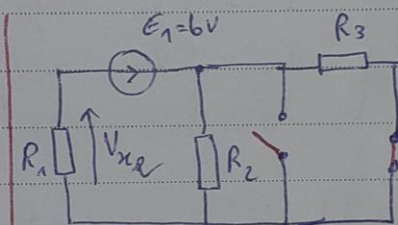

$V_{x2} = -\frac{R_1}{R_1 + R_2} I$

$R_{eq} = R_2 || R_3 = \frac{3 \cdot 6}{3 + 6} = 2\Omega$

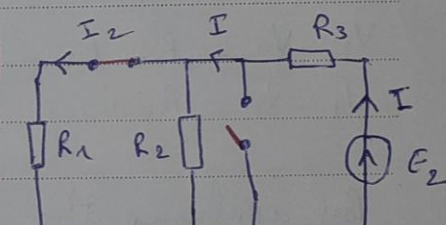$V_{x2} = -\frac{R_1}{R_1 + R_{eq}} I = -2V$



$V_{x3} = R_1 I_2$

$I_2 = \frac{1/R_1}{1/R_1 + 1/R_2} I$

$I_2 = \frac{R_2}{R_1 + R_2} I$

$I = \frac{E_2}{R_{eq}} = \frac{12}{6 + (3 || 1)} = 1.33A$

$V_{x3} = 1.33V$

$V_x = V_{x1} + V_{x2} + V_{x3} = 1.33 - 2 + 1.33$


$V_x = 0.66V$

### Exercise 7:

1. Calculate the potential difference  $U$  between points A and B.

$$U = \frac{\frac{-E_1}{R_1} + \frac{E_2}{R_2} + \frac{0}{R_3} + \frac{0}{R_4}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{\frac{-3}{1} + \frac{12}{2}}{\frac{1}{1} + \frac{1}{2} + \frac{1}{2} + \frac{1}{1}} = 1V$$

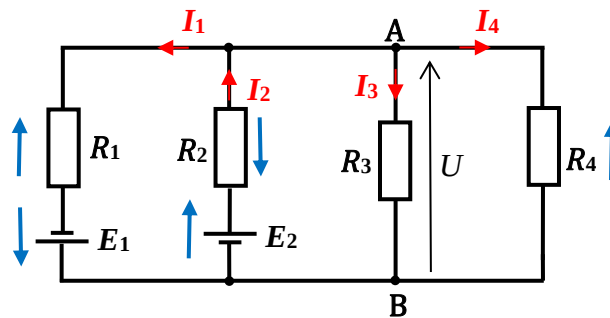2. Calculate and indicate the direction of the current in each resistance.



$$U + E_1 = R_1 I_1 \Rightarrow I_1 = \frac{U + E_1}{R_1} = \frac{1 + 3}{1 \times 10^3} = 4mA$$

$$I_1 = 4mA$$

$$U = E_2 - R_2 I_2 \Rightarrow I_2 = \frac{E_2 - U}{R_2} = \frac{12 - 1}{2 \times 10^3} = 5.5mA$$

$$I_2 = 5.5mA$$

$$U = R_3 I_3 \Rightarrow I_3 = \frac{U}{R_3} = \frac{1}{2 \times 10^3} = 0.5mA$$

$$I_3 = 0.5mA$$

$$U = R_4 I_4 \Rightarrow I_4 = \frac{U}{R_4} = \frac{1}{1 \times 10^3} = 1mA$$

$$I_4 = 1mA$$

3. Check the law of nodes (Kirchhoff's current law).

$$I_2 - I_1 - I_3 - I_4 = 5.5 - 4 - 0.5 - 1 = 0$$



### Exercise 8:

$$r_1 = \frac{R_1 \cdot R_3}{R_1 + R_2 + R_3} ; r_2 = \frac{R_2 \cdot R_3}{R_1 + R_2 + R_3} ; r_3 = \frac{R_1 \cdot R_2}{R_1 + R_2 + R_3}$$

$$r_1 = r_2 = r_3 = \frac{100 \cdot 100}{100 + 100 + 100} = 33,33 \Omega$$

$$I = \frac{E}{R_{eq}} ; R_{eq} = [(r_1 + R_4 + R_5) \parallel (r_2 + R_6) + r_3]$$


$$R_{eq} = 118,17 \Omega ; I = 84,6 \text{ mA}$$

We use the current divider

$$I_e = \frac{\frac{1}{r_1 + R_4 + R_5}}{\frac{1}{r_1 + R_4 + R_5} + \frac{1}{r_2 + R_6}} I = \frac{r_2 + R_6}{r_1 + R_4 + R_5 + r_2 + R_6} I$$

$$I_e = 53,83 \text{ mA}$$

### Exercise 9:

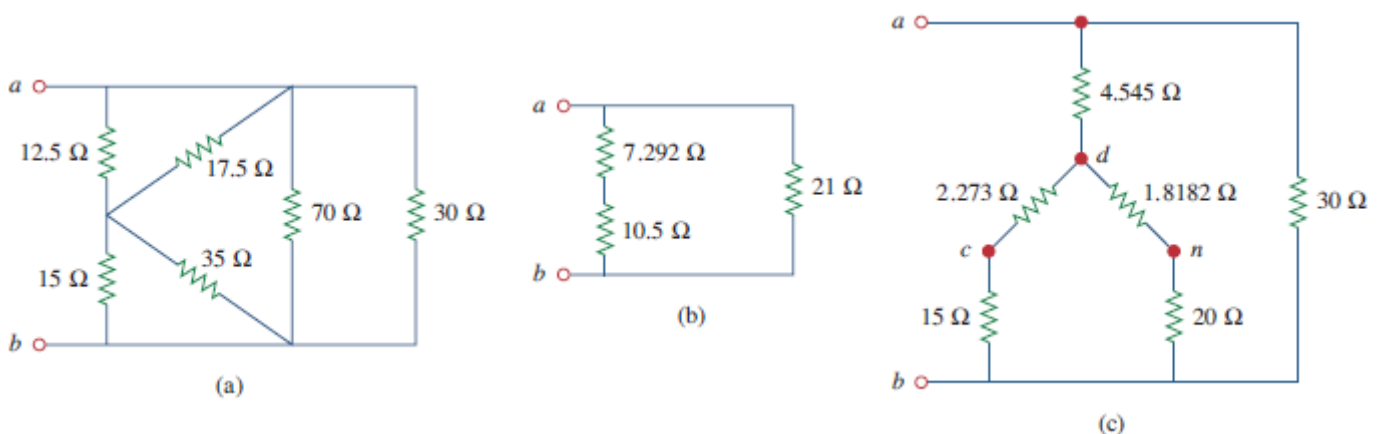

In this circuit, there are two Y networks and three networks. Transforming just one of these will simplify the circuit. If we convert the Y network comprising the 5Ω, 10Ω and 20Ω resistors, we may select

$$R_1 = 10 \Omega, \quad R_2 = 20 \Omega, \quad R_3 = 5 \Omega$$

We have:

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} \\ = \frac{350}{10} = 35 \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \Omega$$

With the Y converted to  $\Delta$ , the equivalent circuit (with the voltage source removed for now) is shown in Figure. (a). Combining the three pairs of resistors in parallel, we obtain

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \Omega$$

$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$

So that the equivalent circuit is shown in Figure. (b). Hence, we find

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$

Then

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 \text{ A}$$

### Exercise 10:

Exercise 10


\* 1] Find the Thevenin equivalent of the circuit.

$V_{Th} = V_{AB} = V_A - V_B$

$V_A = \frac{R_2}{R_1 + R_2} \cdot E = 5 \text{ V}$


$V_B = \frac{R_5}{R_1 + R_4 + R_5} \cdot E = 2.5 \text{ V}$

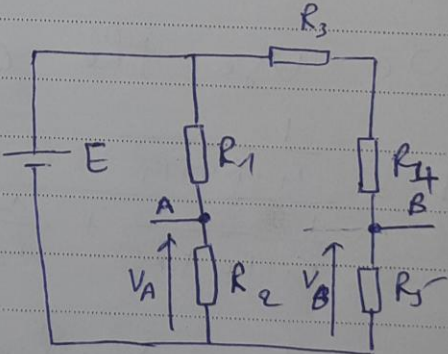$V_{Th} = V_{AB} = V_A - V_B = 5 - 2.5 = 2.5 \text{ V}$






Calculate  $R_{th} = R_{AB}$

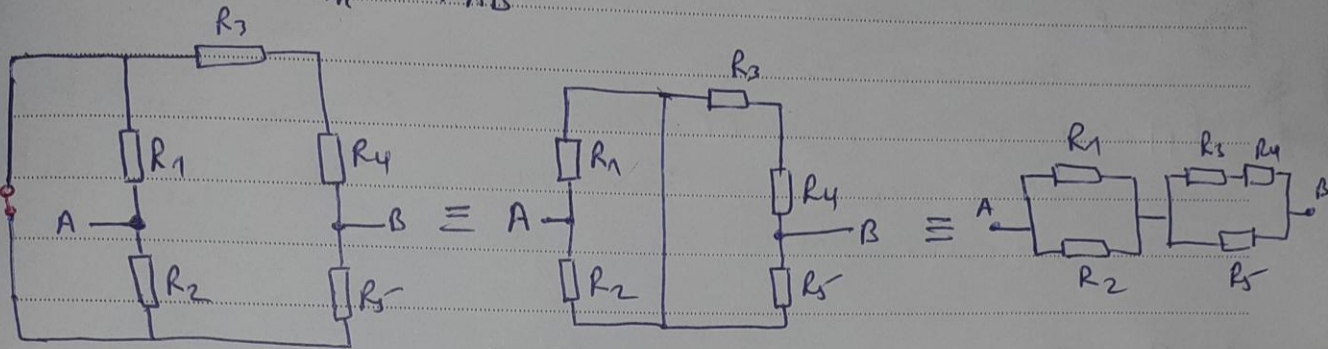


$$R_{th} = R_{AB} = (R_1 \parallel R_2) + [(R_3 + R_4) \parallel (R_5)]$$

$$R_{th} = 68,75 \text{ K}\Omega$$

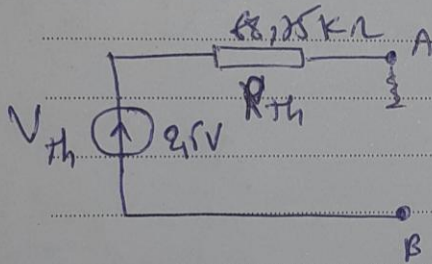

← Thevenin equivalent circuit

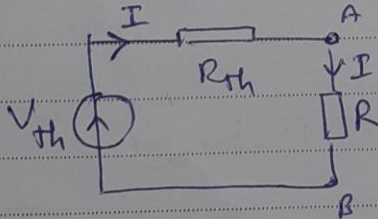
2) Determine the current  $I$  flowing in the resistance  $R$



$$I = \frac{V_{th}}{R_{th} + R} = 14,81 \text{ mA}$$
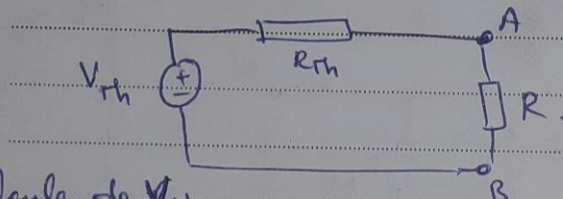
### Exercise 11:

Donner le g n rateur de Th venin. c- -   
M tre le circuit sous la forme suivante



1) Calcul de  $V_{th}$ .

$$V_{th} = V_{AB} = V_A - V_B$$


$$V_A = \frac{R_2}{R_2 + R_1} E_1 = \frac{100}{100 + 200} \cdot 12$$

$$V_A = 8 \text{ V}$$

$$V_B = \frac{R_4}{R_3 + R_4} \cdot E_2 = \frac{100}{100 + 100} \cdot 5$$


$$V_B = 2,5 \text{ V}$$
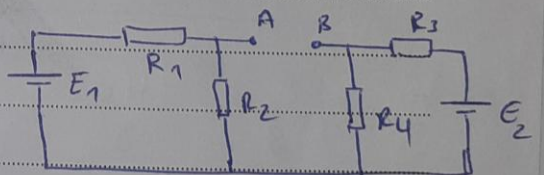
$$V_{th} = V_{AB} = 8 - 2,5 = 5,5 \text{ V}$$





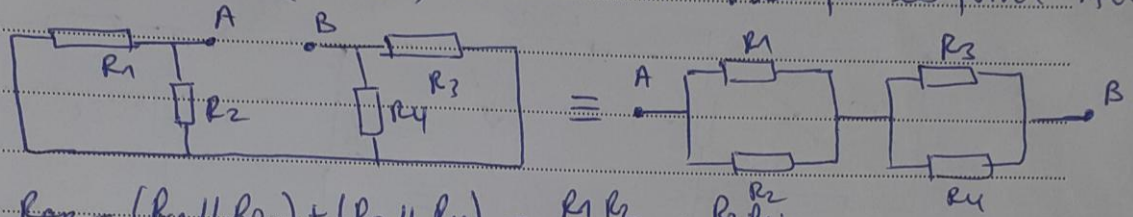
2] Calcul de  $R_{th} (= R_{AB})$ ; la résistance vue par les point A et B



$$R_{th} = R_{AB} = (R_1 \parallel R_2) + (R_3 \parallel R_4) = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$



$$= \frac{100 \cdot 100}{100 + 100} + \frac{100 \cdot 100}{100 + 100}$$


$$R_{th} = 100 \text{ k}\Omega$$

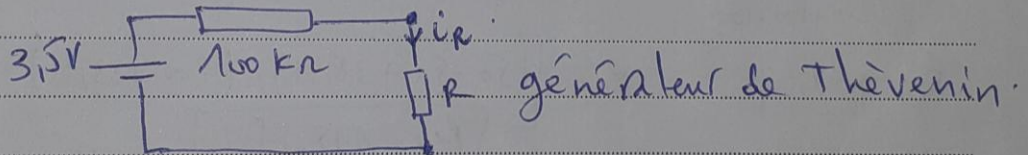

$$I_R = \frac{V_{th}}{R_{th} + R}, \quad V_{AB} = V_R = \frac{R}{R + R_{th}} \cdot E_{th}$$

### Exercise 12:

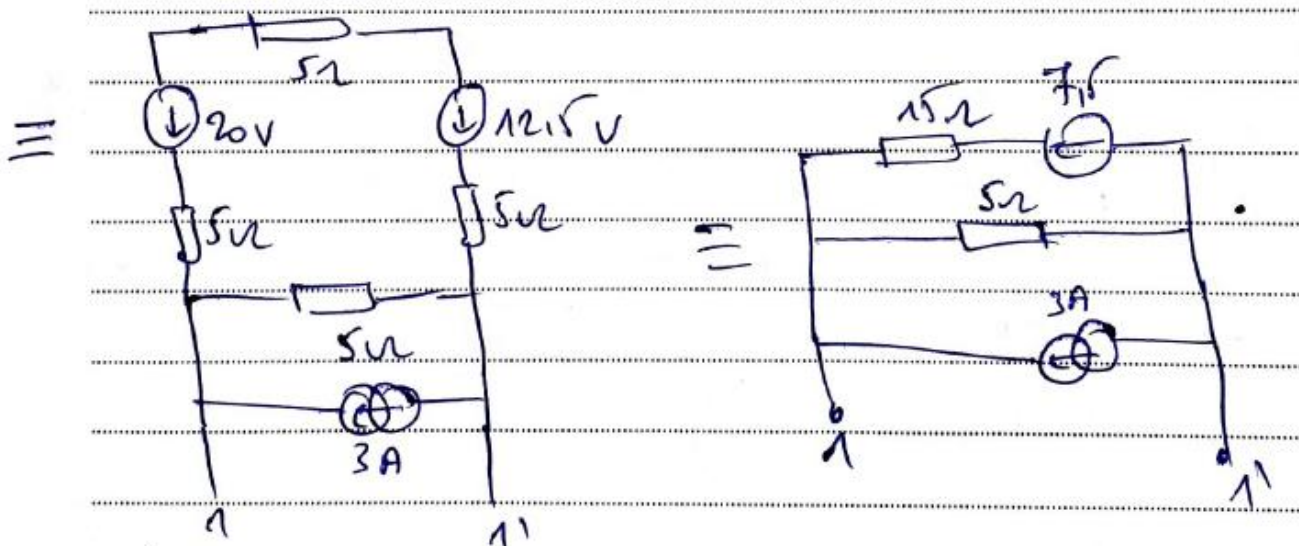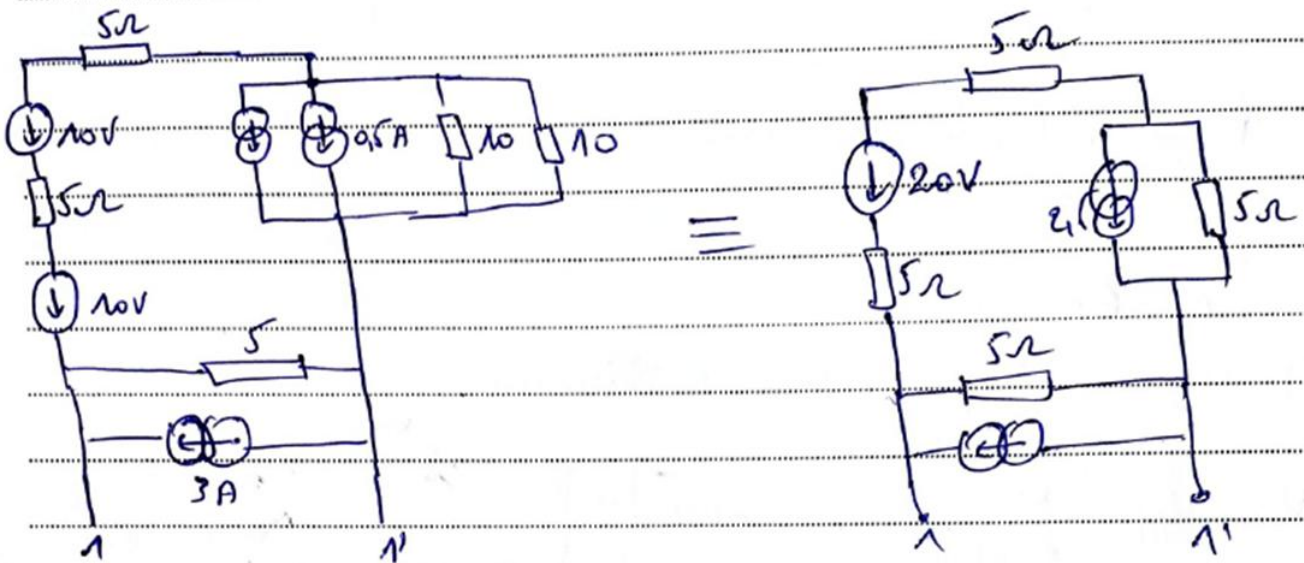

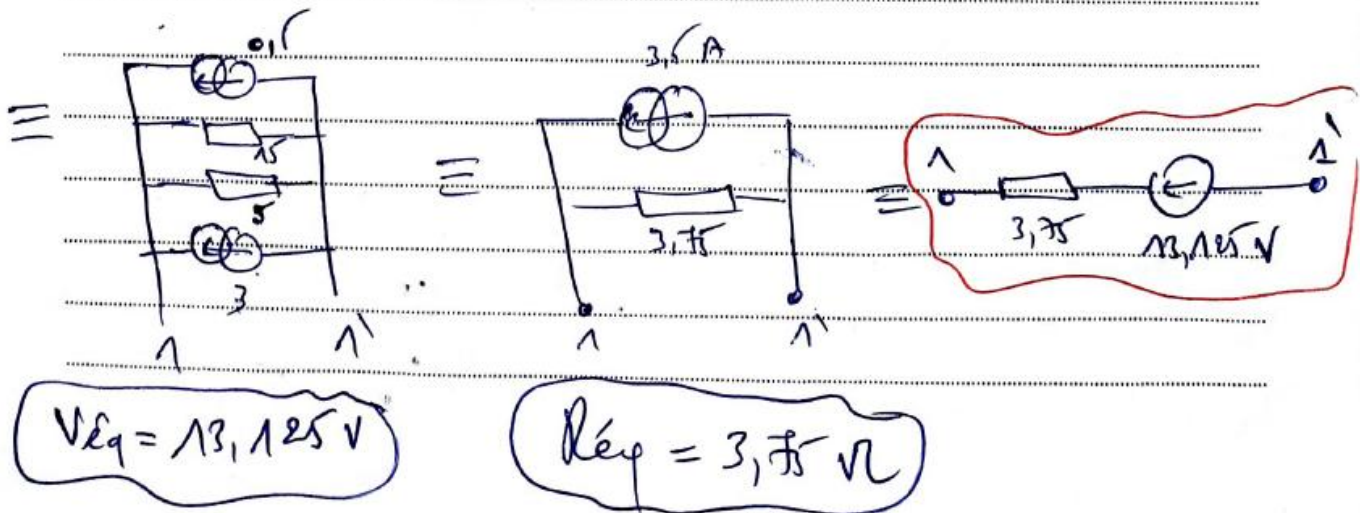

### Exercise 13:

#### 1) Kirchhoff

La loi des nœuds donne:

$$I_1 + I = I_2 \quad \text{--- (1)}$$

La loi des mailles donne:

La maille I donne :  $4 - 16I_1 + 6I = 0 \quad \text{--- (2)}$

La maille II donne :  $4 - 6I - 4I_2 = 0 \quad \text{--- (3)}$


Calculer le courant I

de (2)  $\Rightarrow I_1 = \frac{1}{4} + \frac{3}{8}I \quad \text{--- (4)}$

de (3)  $\Rightarrow I_2 = 6 - \frac{3}{2}I \quad \text{--- (5)}$

Remplaçant (4) et (5) dans (1)  $\Rightarrow$


$$I = 8 \text{ A}$$

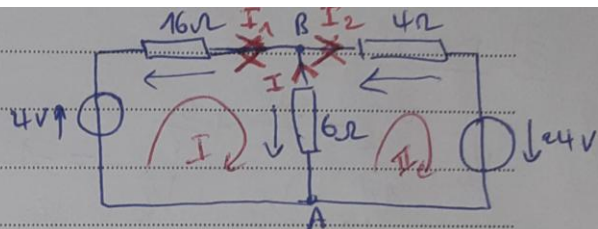

#### 2) Superposition



circuit - 1 -

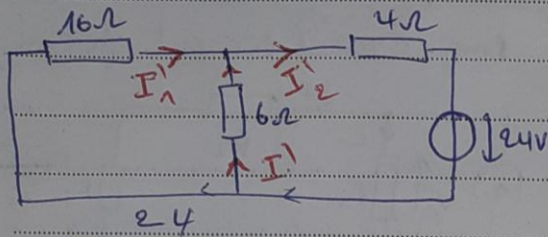

$$I_2' = \frac{24}{(6 \parallel 16) + 4}$$


$$\Rightarrow I_2' = +2,870 \text{ A}$$

On utilise le diviseur de courant:

$$I_1' = \frac{16}{16+6} \cdot 2,870$$

$$I_1' = 2,1087 \text{ A}$$

circuit - 2 -

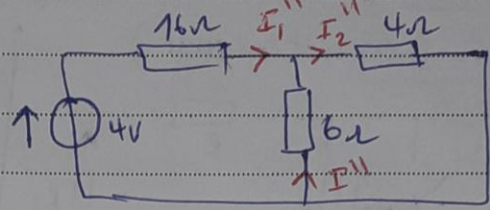

$$I_1'' = \frac{4}{(6 \parallel 4) + 16}$$

$$I_1'' = +0,217 \text{ A}$$

On utilise le diviseur de courant

$$I_2'' = -\frac{4}{4+6} \cdot 0,217$$

$$I_2'' = -0,087 \text{ A}$$

$$I = I' + I'' = 2 \text{ A}$$

### 3) Millman

$$V_B = \frac{\frac{4}{16} - \frac{24}{4} + \frac{0}{6}}{\frac{1}{16} + \frac{1}{4} + \frac{1}{6}} = -12 \text{ V}$$


$$V_{AB} = V_A - V_B$$


$$= 0 - (-12)$$

$$V_{AB} = 12 \text{ V}$$

$$I = \frac{V_{AB}}{6} = \frac{12}{6} = 2 \text{ A}$$

$$I = 2 \text{ A}$$

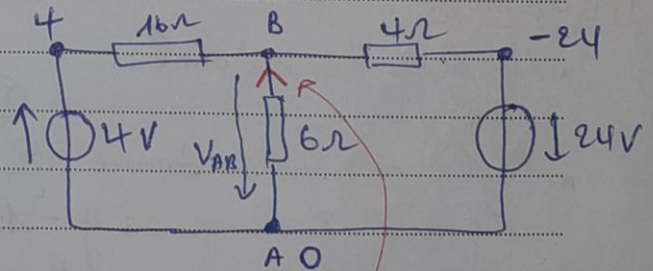

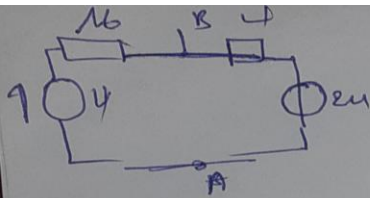

1. Thevenin


$$i = \frac{24 + 4}{16 + 4} = \frac{28}{20} = \frac{14}{10} = 1,4 \text{ A}$$

$$V_B = 4 - 16 \cdot 1,4 = 18,4 \text{ V}$$

$$= 24 - 4 \cdot 1,4$$

$$V_{th} = 14,4$$
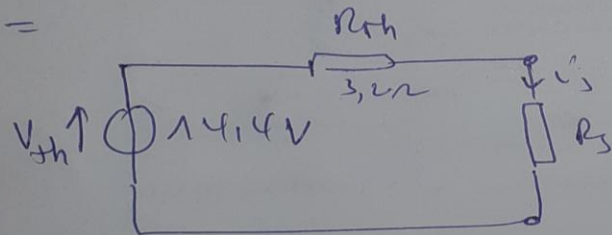
$$R_{th} = \frac{16 \cdot 4}{20} = \frac{64}{20} = \frac{32}{10} = 3,2 \Omega$$



$$i_3 = \frac{18,4}{3,2 + 6} = \frac{18,4}{9,2} = 2 \text{ A}$$