

جامعة محمد بوضياف- المسيلة -
Mohamed Boudiaf University at M'sila

كلية التكنولوجيا
Faculty of Technology
قسم الهندسة الكهربائية و قسم الإلكترونيك

Department of Electrical Engineering and Department of Electronics

University year: 2024/2025

السنة الجامعية: 2025/ 2024

2nd year Electrical Engineering and Electronics

السنة الثانية هندسة كهربائية و إلكترونيك

Applied Work in Electrical Measurement

أعمال تطبيقية في القياسات الكهربائية

PW n° 02: Inductance Measurement

Duration: 1^h30.

Date of the experiment: / /

Report prepared by:

Last Name	First Name	Group	S/Group	Final Note
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-

Instructions :

- Internal laboratory regulations must be observed.
- You must wear a lab coat.
- Attendance is compulsory and will be monitored. Any unjustified absence or failure to hand in a report will result in a mark of 0/20.
- Have your assemblies checked before connecting the voltage source.
- It is strictly forbidden to move equipment from one station to another. In the event of a breakdown or faulty equipment, contact the teacher.
- The report must be written by a maximum of four students.
- The report must be handed in at the beginning of the next session.
- The report must include the following sections:
 - TP cover page.
 - The date of the practical session.
 - Last Name and first name of the main writer.
 - Last Names and first names of the WP participants.
 - Preparation and work in manuscript.

I. Aim of the manipulation

- ✚ Measure an inductance using the volt-amperometric and series RLC methods.
- ✚ Measure Quality factor

II. Equipment used

- ✚ Power Sources (DC).
- ✚ The Oscilloscope
- ✚ Function Generator (GBF)
- ✚ Electrical loads (resistors, inductors and capacitors).
- ✚ Measuring instruments (multimeters, ammeters, milliammeters, voltmeters, millivoltmeters).

III. Evaluation method

- ✚ Continuous assessment: 100%.

IV. Theoretical reminder:

A coil consists of a winding of conductive turns around an insulator. It therefore has a certain internal resistance due to the long length of wire. The coil is therefore symbolised in the receiver convention as follows:

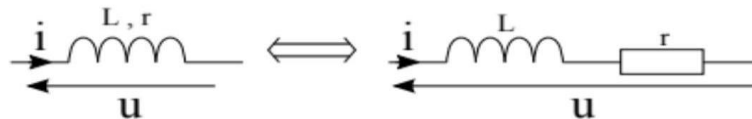


Figure 1: Symbolisation of a real coil, receiver convention.

V. Method n° 01: Indirect measurements using the Volt-Amperometric method

- ❖ Volt-Amperometric method with DC source
- ❖ Carry out the following assembly.

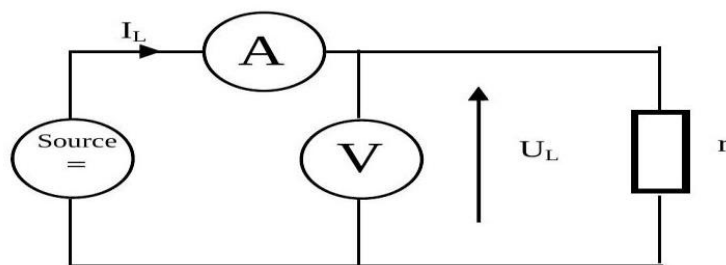


Figure 2: Volt-Amperometric method with DC source

- ❖ Find U_L and I_L by varying U from 1V to 9V.

U(V)	1	3	5	7	9
$U_L(V)$					
$I_L(A)$					
$Z = r = U_L/I_L$					

Table 1

2) Volt-Amperometric method with AC source

- ❖ The coil is fed by a sinusoidal generator $U(t)$ with an effective value $U(t) = 7V$ and a variable frequency.
- ❖ Carry out the installation by positioning the equipment so that $U_L(V)$, I_L

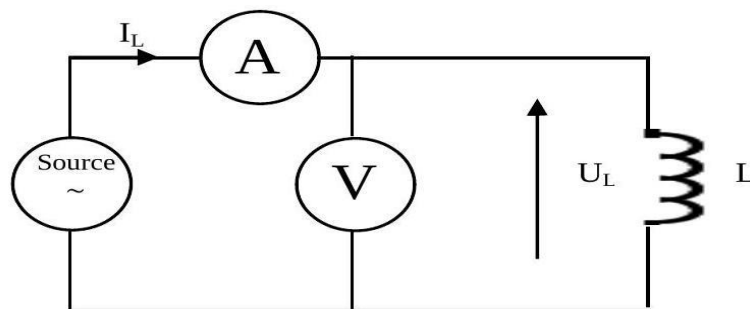


Figure 3: Volt-Amperometric method with AC source

- ✚ Find $U_L(V)$, I_L by varying the frequency from **100 Hz** to **250 Hz**
- ✚ Calculate the value of Z from these measurements,
- ✚ Derive L

f(Hz)	100	150	200	250
$U_L(V)$				
$I_L(A)$				
$Z = U_L/I_L$				
L				

Table 2

VI. Method n°02 : Indirect measurements using the Resonance of a series RLC circuit.

- ❖ The Resonance of a series RLC circuit

To study the resonance of the RLC circuit, we will make the following series circuit:

- ❖ An inductor set at **150mH**
- ❖ A capacitor set at **3.3 μ F**
- ❖ A resistor set at **560 Ω** .

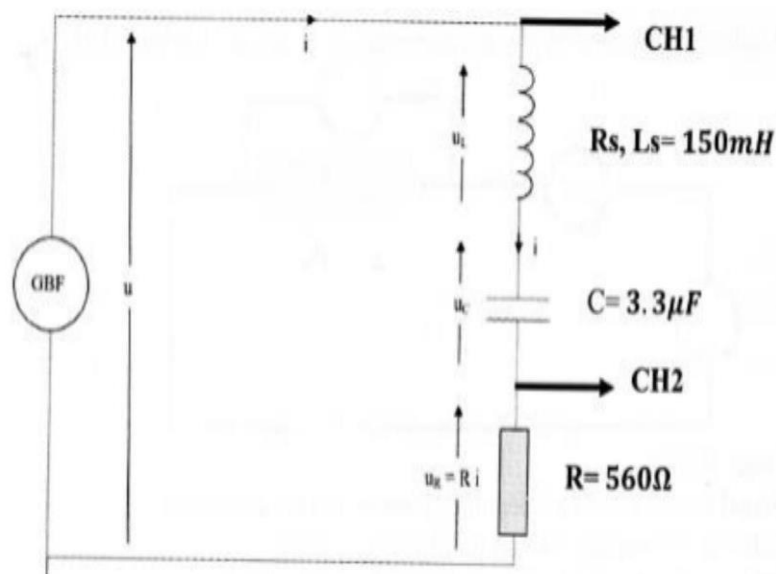


Figure 4: RLC circuit

- ✚ Look at the current and voltage curves on the oscilloscope. *
- ✚ Plot these curves on a millimetre sheet,
- ✚ Calculate the phase shift $\varphi_{\text{experimental}}$ directly on the oscilloscope and compare it with the theoretical value.
- ✚ In general the impedance Z of a dipole is given by the relationship: $Z = U_{\text{max}} / I_{\text{max}} = U_{\text{eff}} / I_{\text{eff}} = U / I$ through the dipole.
- ✚ Record the amplitude of the voltage across the resistor U_R , the capacitor U_C and the coil U_L and the current I for frequencies between **100 Hz** and **500 Hz**.
- ✚ Plot the curves $I, U_C, U_L, U_R = G(f)$
- ✚ Calculate the resonance frequency
- ✚ Calculate the bandwidth and the quality factor, given that $Q = f_0 / \Delta f$
- ✚ Deduce the value of L for all frequencies;
- ✚ Discuss each of the results obtained.

f(Hz)	100	200	f_0	250	500
I(A)					
U_R(V)					
U_C(V)					
U_L(V)					
Z = U/I					
R = U_R/I					
Z_C = U_C/I					
Z_L = U_L/I					
L					

Table 3

2) Interpretation of results

VII. Conclusion

