

First Series of Exercises : **Continuous regime and fundamental theorems**

Exercise 1: (Kirchhoff's laws)

Consider the circuit in Figure 1:

- 1- Determine the number of **nodes**, the number of **branches**, as well as the number of possible **meshes**.
- 2- By applying **Kirchhoff's laws**, write the equations of the meshes.
- 3- Determine the current intensities in the three branches. Knowing that : $R_1 = 2\Omega$, $R_2 = 5\Omega$, $R_3 = 10\Omega$, $E_1 = 20V$, $E_2 = 70V$

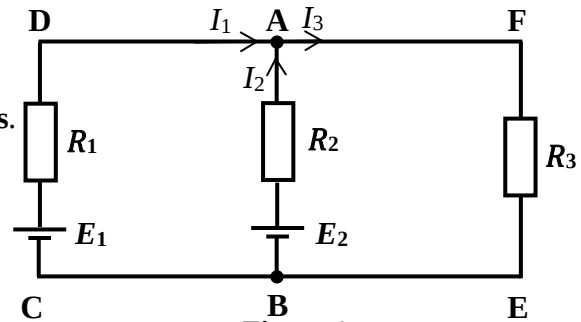


Figure 1

Exercise 2 : (Current divider)

From the circuit in figure 2, determine:

- 1- The equivalent resistance seen from points **a** and **b**.
 - 2- The current supplied by source V_f .
 - 3- The current flowing through each of the resistors R_1 and R_2 .
- $V_f = 18V$, $R_1 = 7\Omega$, $R_2 = 2\Omega$.

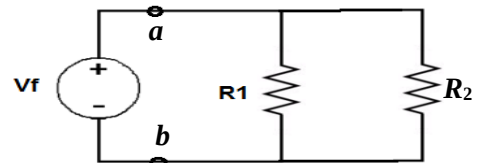


Figure 2

Exercise 3 : (Voltage divider)

By applying the voltage divider, determine the current i and the voltage u .

$E = 6V$, $R_1 = 100\Omega$, $R_2 = R_3 = R_4 = 50\Omega$.

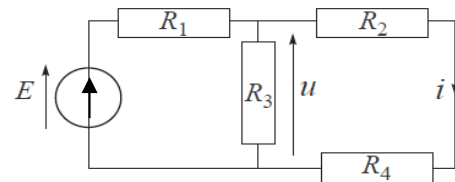


Figure 3

Exercise 4 : (Current/Voltage dividers)

- 1- Use the **voltage divider theorem** to calculate the voltages V_1 and V_2 in the case of Figure 4.
 - 2- Use the **current divider theorem** to calculate the currents I_1 , I_2 , I_3 , and I_4 in Figure 5.
- Data : $E = 3V$, $I = 5A$, $R_1 = R_3 = 1\Omega$, $R_2 = R_4 = 2\Omega$.

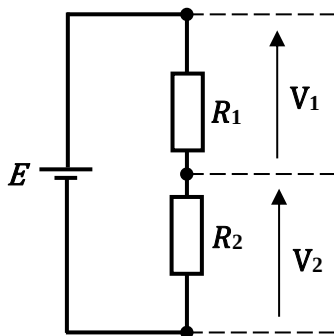


Figure 4

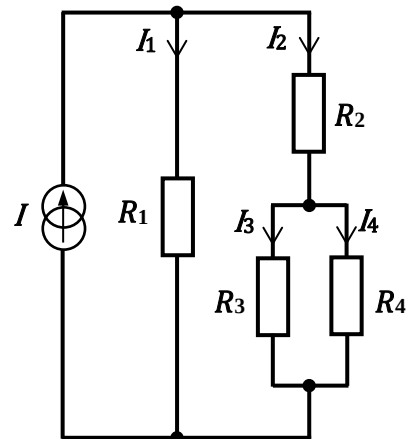


Figure 5

Exercise 5 : (Superposition Theorem)

Using the **superposition theorem**, determine the voltage across resistor R_1 .

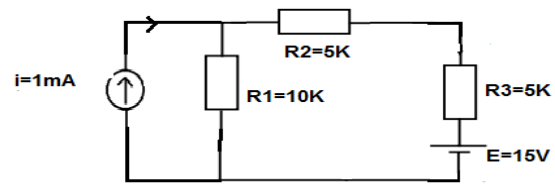


Figure 6

Exercise 6 : (Superposition Theorem)

In figure 7, calculate the voltage V_x by using the **superposition principle**.

Data : $E_1 = 6V$, $E_2 = 12V$, $I = 2A$,
 $R_1 = 1\Omega$, $R_2 = 3\Omega$, $R_3 = 6\Omega$.

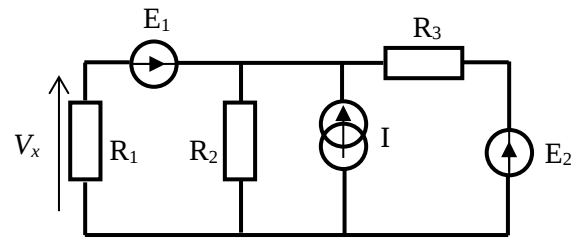


Figure 7

Exercise 7 : (Millman's Theorem)

Applying **Millman's theorem**

1. Calculate the potential difference U between points A and B.
2. Calculate and indicate the direction of the current in each resistance.
3. Check the law of nodes (Kirchhoff's current law).

With : $E_1 = 3V$, $E_2 = 12V$, $R_1 = R_4 = 1k\Omega$, $R_2 = R_3 = 2k\Omega$

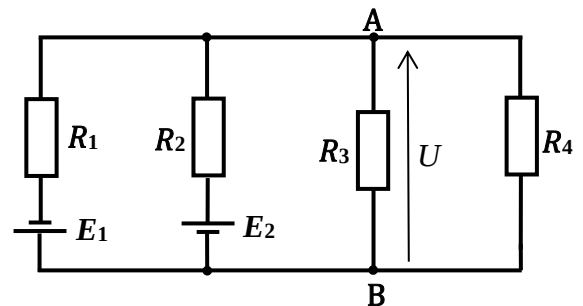


Figure 8

Exercise 8: (Kennelly transformations)

Consider the circuit shown in figure 9.

- Calculate the values of currents I and I_l .

$E = 10V$, $R_1 = R_2 = R_3 = 100\Omega$, $R_4 = R_5 = 50\Omega$, $R_6 = 200\Omega$,

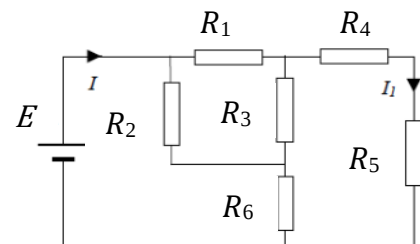


Figure 9

Exercise 9: (Kennelly transformations)

Obtain the equivalent resistance R_{ab} for the circuit in figure 10 and use it to find current i .

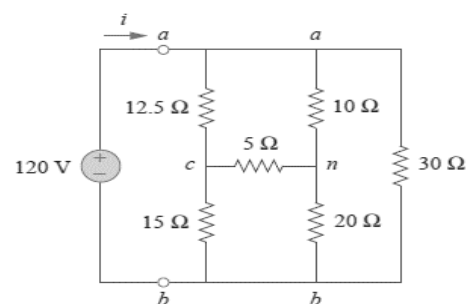


Figure 10

Exercise 10: (Thevenin's Theorem)

- Find the **Thevenin** equivalent of the circuit in figure 11, without taking into account the resistance R .
- Determine the current I flowing in the resistance R

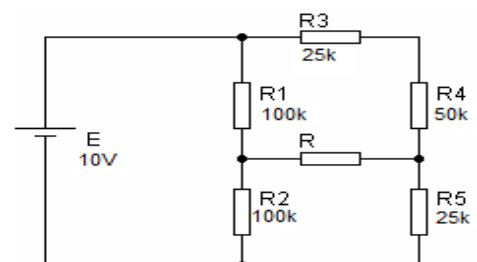


Figure 11

Exercise 11: (Thevenin's Theorem)

Using the **Thevenin's theorem**,

- Determine the voltage across resistor R .
- Determine the current I flowing in the resistance R

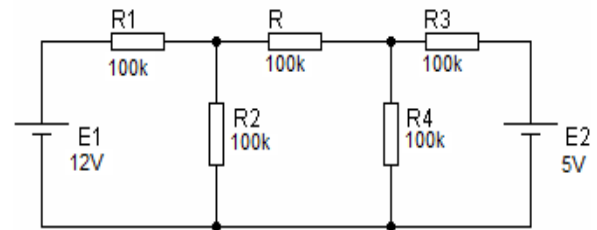


Figure 12

Exercise 12: (Equivalence Thevenin-Norton)

- 1- Reduce the circuit in the figure opposite to an equivalent Dipole comprising a voltage source V_{eq} in series with a resistor R_{eq} .

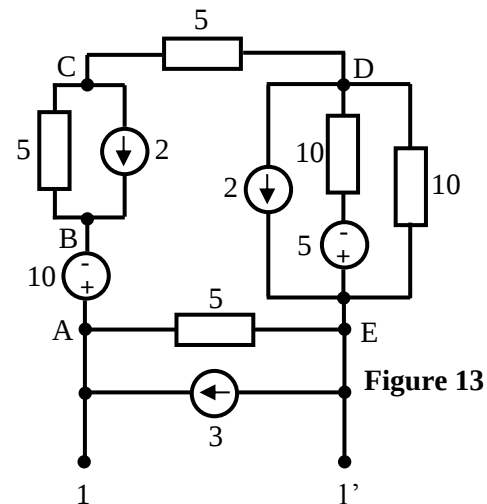


Figure 13

Exercise 13: (Kirchhoff / Superposition/ Millman/thévenin)

Calculate the current intensity in branch AB by applying:

1. The Kirchhoff's laws.
2. The superposition theorem.
3. The Millman's theorem.
4. the Thevenin's theorem.


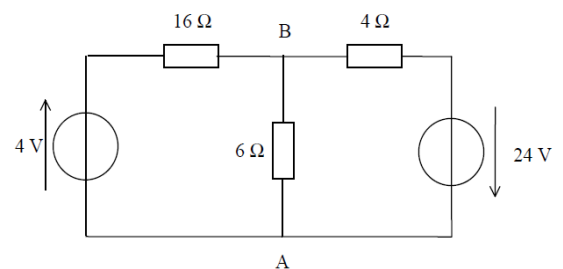
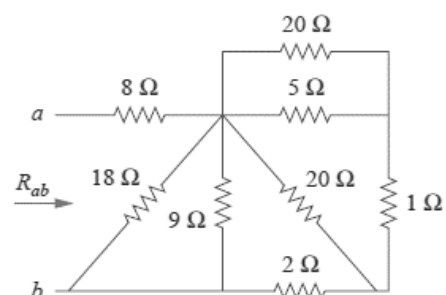


Figure 14

Additional exercises

Exercise 1:

Calculate the equivalent resistance R_{ab} in the following circuits:

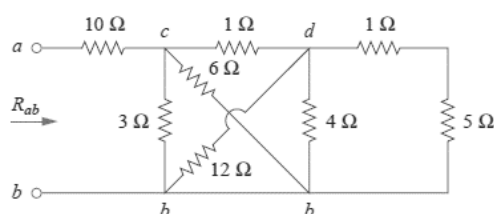


Exercise 2:

In the opposite circuit:


- 1- Calculate UEF,
- 2- Calculate the current intensity I_0 .
- 3- Calculate the intensity I' flowing in the branch containing the generator E' (specify its directions).
- 4- Calculate the intensities i_1 , i_2 and i_3 .

Data : $R = 1\Omega$, $E = 5V$ and $E' = 3V$.

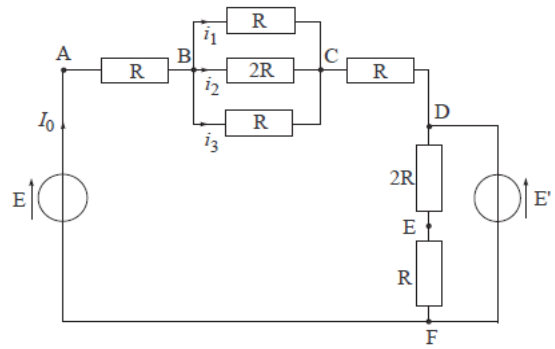

Exercise 3:


Determine the currents of the meshes i_1 and i_2 in the following circuit:

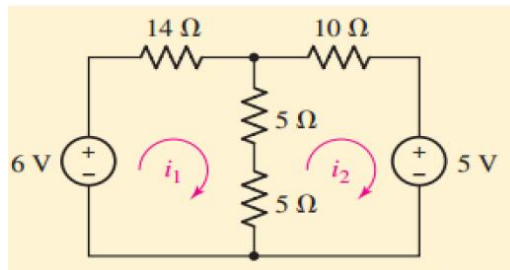

Exercise 4:

The circuit includes three generators ($E_1 = 20V$, $R_1 = 3\Omega$, $E_2 = 15V$, $R_2 = 4\Omega$, $E_3 = 8V$, $R_3 = 5\Omega$).


- Determine the value of the current intensity in R_3 by applying the **superposition theorem**.

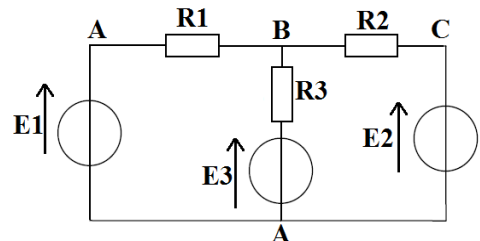

Exercise 5:

Consider the electrical circuit in Figure 1, We give the following element values: $R_1 = 2K\Omega$, $R_2 = 4K\Omega$, $R = 2K\Omega$, $E_1 = 20V$ et $E_2 = 10V$.

- 1- Calculate the elements of the **Thévenin** generator (V_{Th} and R_{Th}) seen between terminals A and B (without taking into account the resistance R).
- 2- Determine the **Norton** generator (I_N and E_N) seen between terminals A and B.
- 3- Determine the current I in branch AB.

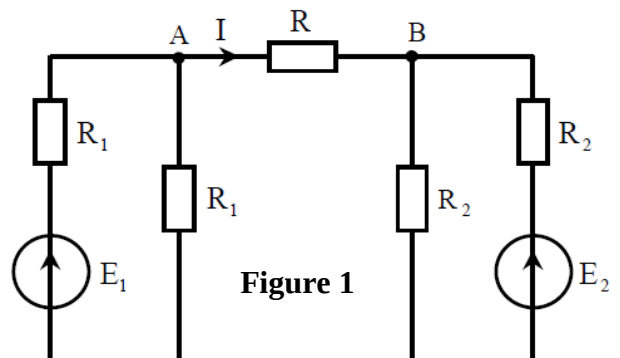

Exercise 6 :

Determine the **Thévenin** generator of the figure 2, without taking into account the resistance R.

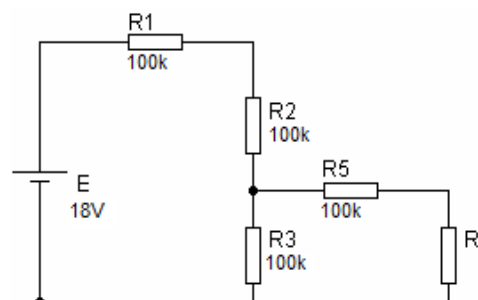


Figure 2