


Series N°3: Single-phase circuits and electrical powers

Exercise 01

Consider the electrical circuit shown in Fig 1, the source current and voltage are:


$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \text{ And } v(t) = 15 \sin(314t + \frac{5\pi}{6})$$

1. Calculate the equivalent impedance $\underline{Z}$ seen by the source.
2. Give the numerical values of: R , L and Z .
3. Calculate the powers of the circuit: active(real) power P , reactive power Q and apparent power S relative to this circuit.
4. Draw the power triangle of the circuit and specify the power factor.

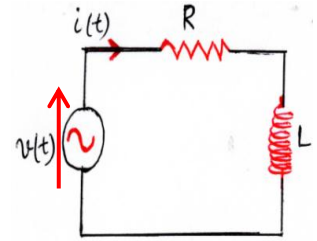

Exercise 02


Calculate the equivalent impedance $\underline{Z}_{AB}$ between the two points A and B.

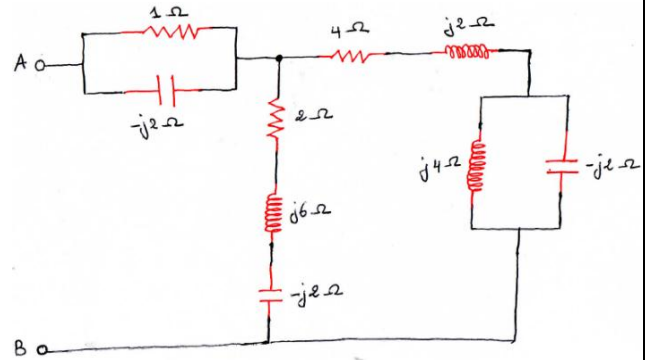

Exercise 03

Consider the single-phase circuit shown in Figure 3, supplied by a sinusoidal AC voltage source.

1. Write, in complex (phasor) form, the expressions of the current $\underline{I}_1$, $\underline{I}_2$ and $\underline{I}$ for the given circuit.
2. Determine the equivalent impedance $\underline{Z}_{eq}$ seen by the source.
3. Find the phasor expression of the voltage across the capacitor $\underline{V}_C$.
4. Calculate the real power P , the reactive power Q and the complex power $\underline{S}$ associated with the circuit.

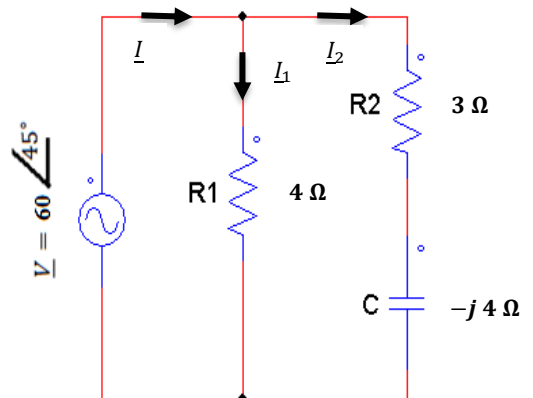

Exercise 04

A single-phase electrical installation, supplied by **220 V / 50 Hz** comprises:

- **Ten 100 W** lamps;
- A **1,5 kW** electric radiator;
- Three identical electric motors, each absorbing a power of **2 kW** with a power factor of **0.70**.

These different devices operate simultaneously.


- 1- What are the active and reactive powers consumed by the installation?
- 2- What is its power factor?
- 3- What is the rms current in the line cable?

Exercise 05:

Consider the circuit in fig 4, supplied by a sinusoidal voltage source:

$$v(t) = 100 \sin(5000t + 45^\circ)$$

1. Calculate the current in each branch ($i_R(t)$, $i_C(t)$ et $i_L(t)$).
2. Derive the expression for the total current $i(t)$ delivered by the source.
3. Calculate the equivalent impedance of the circuit.
4. Compute the electrical powers using the RMS quantities: active, reactive and apparent power consumed by the circuit.

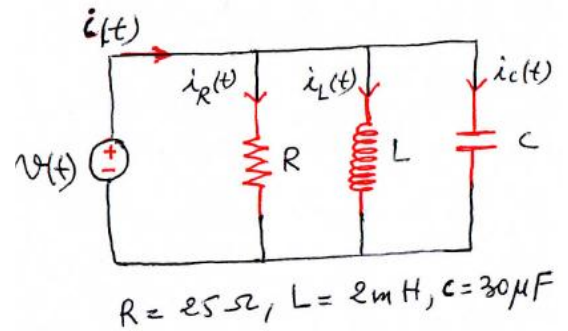

Exercise 06


Consider the circuit shown in the figure 5

The source voltage is a sinusoidal signal whose phasor (RMS) is $\underline{V}$. with magnitude $V = 100V$ at frequency ($f = 50 \text{ Hz}$).

All circuit elements are given directly by their complex impedances (use $\underline{Z}$ values as shown on the schematic).

The components of the circuit are directly characterized by the value of their complex impedance.

- 1) Calculate the effective value of the current.
- 2) Calculate the phase of the current if we consider the voltage at the origin of the phases. Then write the instantaneous expressions of v and i .
- 3) Write the KVL that governs the circuit and give its vector diagram.

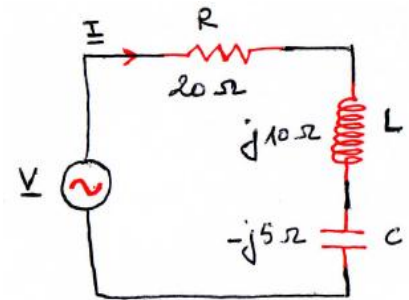

Exercise 07

The voltages at the terminals of each impedance are given in fig 6.

$$v_1(t) = 70.7 \sin(\omega t + 30^\circ) [V]$$

$$v_2(t) = 28.3 \sin(\omega t + 120^\circ) [V]$$

$$v_3(t) = 14.14 \cos(\omega t + 30^\circ) [V]$$

1. Find the expression of $v_T(t)$ and $i(t)$.
2. Calculate the equivalent impedance of the circuit.
3. Give the voltmeter reading.

