

**RECITATION 06**

**Exercise 01**

A 11kV, 30MVA generator has  $x_1=x_2=0.2\text{pu}$  and  $x_0=0.05\text{pu}$ . a line to ground fault occurs on the generator terminal. Find the fault current and line to line voltages during fault conditions. Assume that the generator neutral is solidly grounded.

**Exercise 02:**

The single line diagram is drawn in figure 1. Before the occurrence of a solid L-G fault at line g the motors were loaded. If the prefault current is neglected, calculate the fault current and sub transient currents in all parts of the system.



Figure 1: Single-line diagram the system

**Exercise 03:**

Two 11kV, 12 MVA, 3 ph, star connected generators operate in parallel figure 2. The positive, negative and zero sequence reactance of each being  $j0.09$ ,  $j0.05$  and  $j0.04$  pu respectively. A single line to ground fault occurs at the terminals of one the generators.:

1. Draw the positive, negative and zero sequences
2. Estimate The fault current
3. Estimate Current in grounding resistor
4. Estimate Voltage across grounding resistor

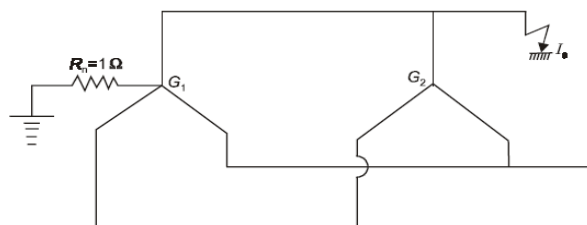


Figure 2: Circuit connection of two generators