



Exercise 1: (05 points)

- 1- Calculate, using triple integration, one sixth ($1/6$) of the volume enclosed between two coaxial cylinders (as shown in **Figure 1**), whose radii are $R1$ and $R2$ with $R1 < R2$, and whose common height is h . (03 points)
- 2- Prove that the resultant of two vectors can be expressed by the relation:

$$V = \sqrt{V_1^2 + V_2^2 + 2 V_1 V_2 \cos \theta}$$

where V is the magnitude of the resultant vector, $V1$ and $V2$ are the magnitudes of the two vectors, and θ is the angle between $\vec{V}_1$ and $\vec{V}_2$. (02 points)

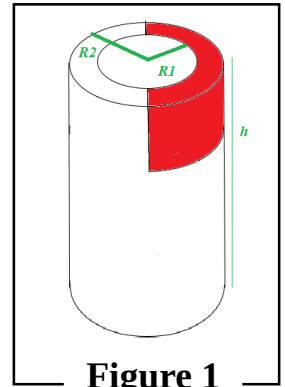


Figure 1

Exercise 2 (05 points)

Consider an infinite plane that carries a surface charge distribution with density σ , $\sigma > 0$. **Figure 2**

- 1- Using Gauss's theorem, find the expression of the electrostatic field $\vec{E}(r)$ at any point in space. (03 points)
- 2- Deduce the expression of the electric potential $V(r)$ at any point in space. (1,5 points), (0,5 points) for the representation.

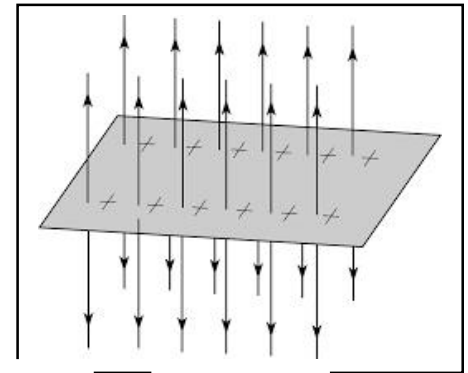


Figure 2

Exercise 3: (05 points)

Consider a planar orthonormal coordinate system (x, O, y) (**Figure 3**). At point **A**, a charge $q_A = -q$ is placed; at point **B**, a charge $q_B = +2q$; at point **C**, a charge $q_C = +3q$; and at point **D**, a charge $q_D = -2q$. The distances are $OA = OB = OC = OD = a = 5 \text{ cm}$, and $q = 10^{-9} \text{ C}$. Take $k = 9 \times 10^9 \text{ SI}$.

1. Determine the total electric potential V_O at point **O** and calculate its value. (01 point)
2. Determine the total electric field vector $\vec{E}_O$ at point **O** and calculate its magnitude. (1,5 points)
3. A charge $q' = -q/2$ is placed at point **O**. Determine the resultant force acting on the charge q' . (0,5 points)
4. Determine the total electric field vector $\vec{E}_D$ at point **D**. (02 points)

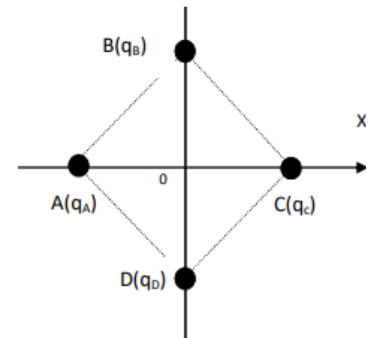


Figure 3

Exercise 4: (05 points)

Consider the circuit shown in the following figure (**Figure 4**).

5. Determine the equivalent resistance R_{AB} between points **A** and **B** of the circuit. (1,5 point)
- Points **A** and **B** are then connected to a source of electromotive force $E = 56 \text{ V}$, with negligible internal resistance.
6. Calculate the current I supplied by the source, specifying the direction of current flow. (0,5 points)
 1. Determine the potential difference V_{AC} between points **A** and **C**, and hence deduce the current in branch **CD**. (1,5 point)
 2. Determine the potential difference V_{EF} between points **E** and **F**, and hence deduce the current in branch **EF**. (1,5 points)


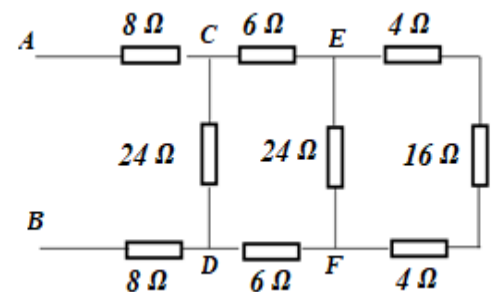


Figure 4

التمرين 1

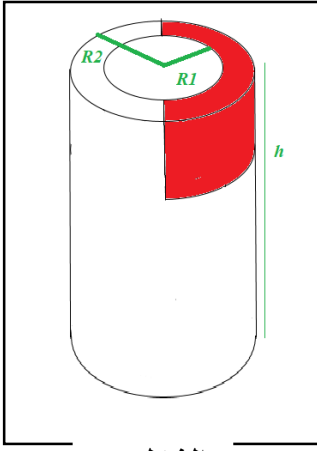

الشكل 1

- احسب، باستعمال التكامل الثلاثي، سدس (1/6) الحجم المحصور بين أسطوانتين متحدتي المحور (كما هو موضح في الشكل 1)، نصفي قطريهما $R1$ و $R2$ حيث $R1 < R2$ وارتفاعهما h
- أثبت أن محصلة شعاعين يمكن التعبير عنها بالعلاقة التالية:

$$V = \sqrt{V_1^2 + V_2^2 + 2 V_1 V_2 \cos \theta}$$

حيث أن V يمثل طول شعاع المحصلة، و $V1$ و $V2$ يمثلان طويلتي الشعاعين، و θ هي الزاوية المحصورة بين الشعاعين $\vec{V}_1$ و $\vec{V}_2$

التمرين 2

نعتبر صفيحة لا نهائية مشحونة سطحياً بتوزيع شحني سطحي σ ($\sigma > 0$). أنظر الشكل 2.

- احسب الحقل الكهربائي $\vec{E}(r)$ في جميع نقاط الفضاء باستخدام نظرية غوص. (يطلب التمثيل)
- احسب الكمون الكهربائي $V(r)$ في جميع نقاط الفضاء باستخدام نظرية غوص.

التمرين 3

نعتبر معلماً متعامداً ومتجانساً ومستوياً (x, O, y) (الشكل 3). توضع عند النقطة A شحنة كهربائية مقدارها $q_A = -q$ ، وعند النقطة B شحنة مقدارها $q_B = +2q$ ، وعند النقطة C شحنة مقدارها $q_C = +3q$ ، وعند النقطة D شحنة مقدارها $q_D = -2q$. المسافات هي:

$$q = 10^{-9} \text{ C}, \text{ حيث } OA = OB = OC = OD = a = 5 \text{ cm}$$

- أوجد الكمون الكهربائي الكلي V_O عند النقطة O، ثم أحسب قيمته العددية.
- أوجد شعاع الحقل الكهربائي الكلي $\vec{E}_O$ عند النقطة O، ثم أحسب طويلته.
- توضع شحنة $q' = -q/2$ عند النقطة O، أوجد محصلة القوة المؤثرة على الشحنة q' .


4. أوجد شعاع الحقل الكهربائي الكلي $\vec{E}_D$ عند النقطة D

$$k = 9 \times 10^9 \text{ SI}$$

التمرين 4

نعتبر الدارة الكهربائية الموضحة في الشكل التالي (الشكل 4).

- أحسب المقاومة المكافئة R_{AB} بين النقطتين A و B في الدارة. يتم توصيل النقطتين A و B بمصدر قوة دافعة كهربائية (مولد) $E = 56 \text{ V}$ ، مع إهمال المقاومة الداخلية للمصدر.
- أحسب التيار I الذي يمدّه المصدر، مع تحديد اتجاه تدفق التيار.
- حدد فرق الكمون V_{AC} بين النقطتين A و C، ومن ثم أحسب التيار في الفرع CD.
- حدد فرق الكمون V_{EF} بين النقطتين E و F، ومن ثم أحسب التيار في الفرع EF.

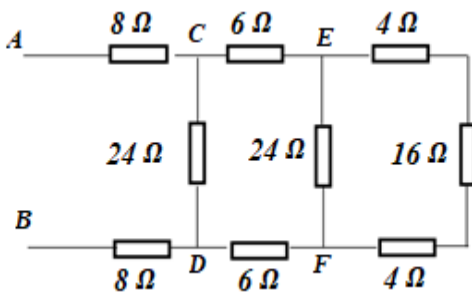

الشكل 4